


Ch 5. Synchronous sequential logic

5.1 Introduction

- In order to perform useful or flexible sequences of operations, we need to be able to construct circuits that can store information between the operations.
- latches and Flip-Flops
- Sequential circuits consisting of both flip-flop and combinational logic

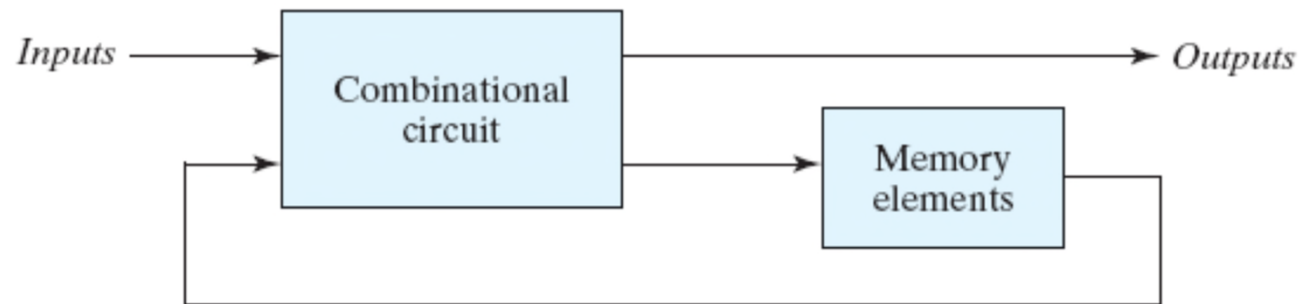
5.2 Sequential circuits

- Outputs are function of inputs and present states
- Present states are supplied by memory elements



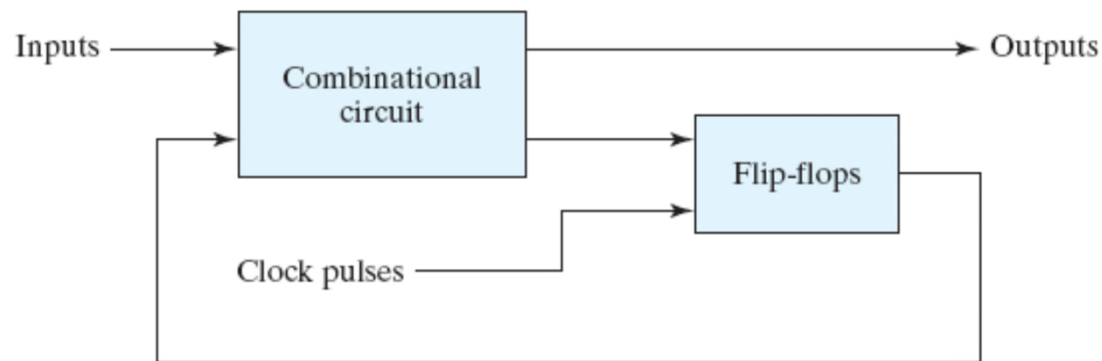5.2 Sequential circuits

- Two types of sequential circuit
- Synchronous : behavior depends on the signals affecting storage elements at discrete time
- Asynchronous : behavior depends on inputs at any instance of time



(a) Block diagram



(b) Timing diagram of clock pulses

5.3 Latches

SR

- 2

NOR

NAND

- SR latch : consist of two cross-coupled NOR gates
- $S=1, R=0$ then $Q=1$ (set)
- $S=0, R=1$ then $Q=0$ (reset)
- $S=0, R=0$ then no change (keep condition)
- $S=1, R=1$ $Q=Q'=0$ (undefined)

 


Fig. 5-3 SR Latch with NOR Gates

5.3 Latches - SR latch

- S'R' latch with NAND gates
 - Require the complement value of NOR latch

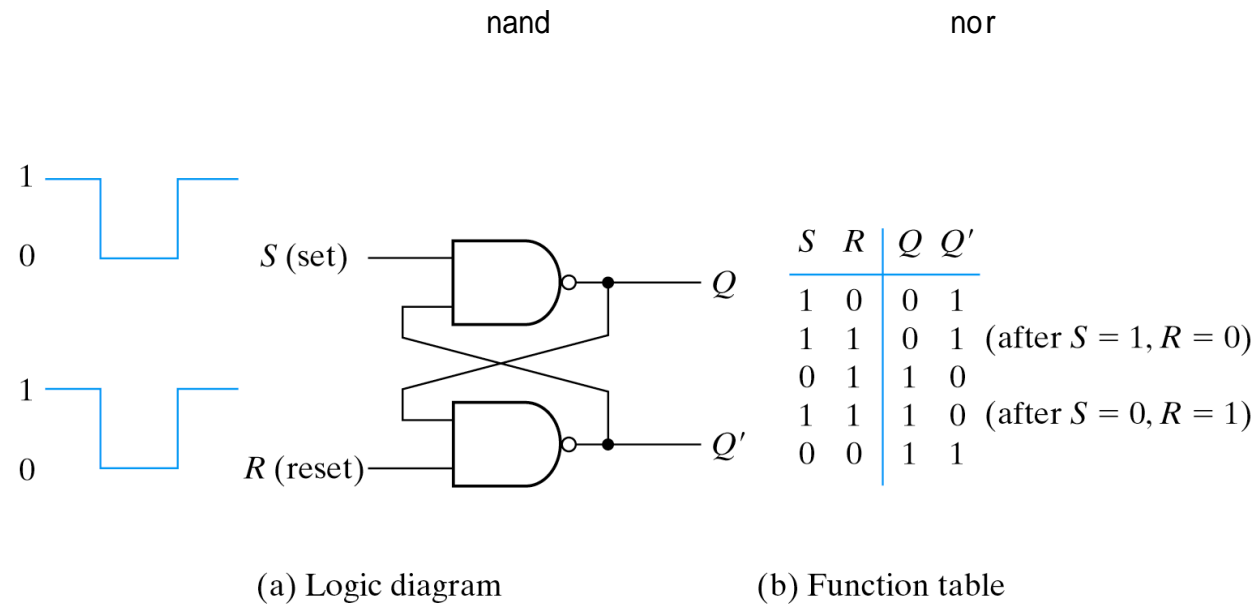



Fig. 5-4 SR Latch with NAND Gates

○ L □ ○

 5.3 Latches - SR latch

● SR latch with control input


- Add two NAND gate and control signal
- $C=0$ (no action), $C=1$ (act as SR latch)



(a) Logic diagram


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

 

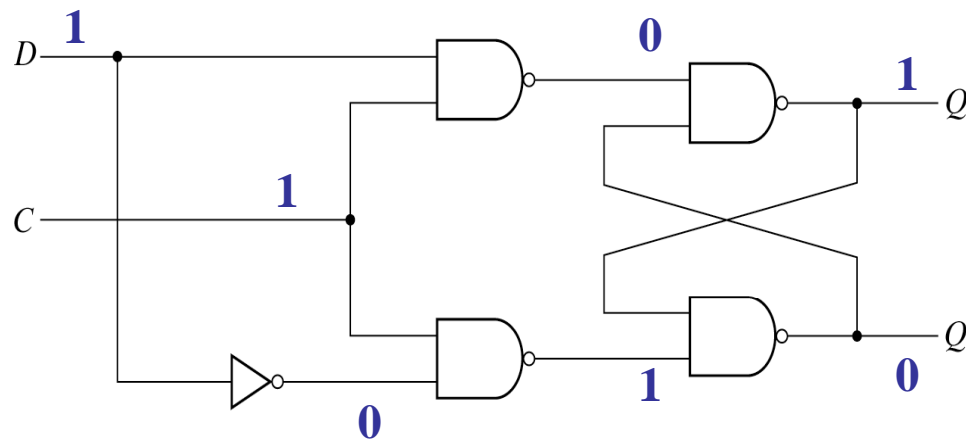5.3 Latches - D latch

- Eliminate indeterminate state in SR latch
 - $C=1$, output value is equal to D




(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	$Q = 0$; Reset state
1	1	$Q = 1$; Set state


(b) Function table

Fig. 5-6 D Latch

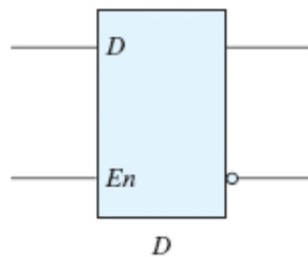

5.4 Latch Timing Problem In Synchronous Circuit

- Consider the following circuit:

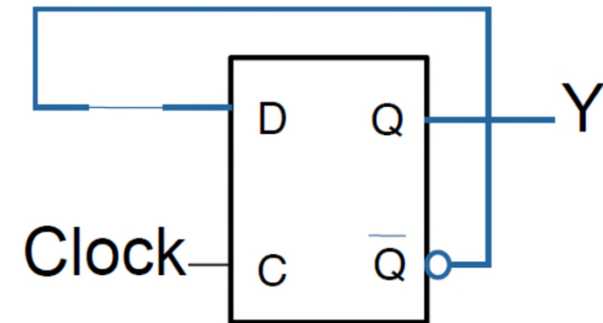

- Desired behavior: Y changes only once per clock pulse
- As long as $C = 1$, the value of Y continues to change!



→ This behavior is clearly unacceptable.

5.4 Flip-Flops

- Latch : case (a), output changes as input changes
- Flip-flop : output only changes at clock edge



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response

5.4 Flip-flops – Master-Slave Flip-Flop

- Negative edge triggered D flip-flop
- $C=0$: master disable, slave enable
- Output has no relation with input
- $C=1$: master enable, slave disable


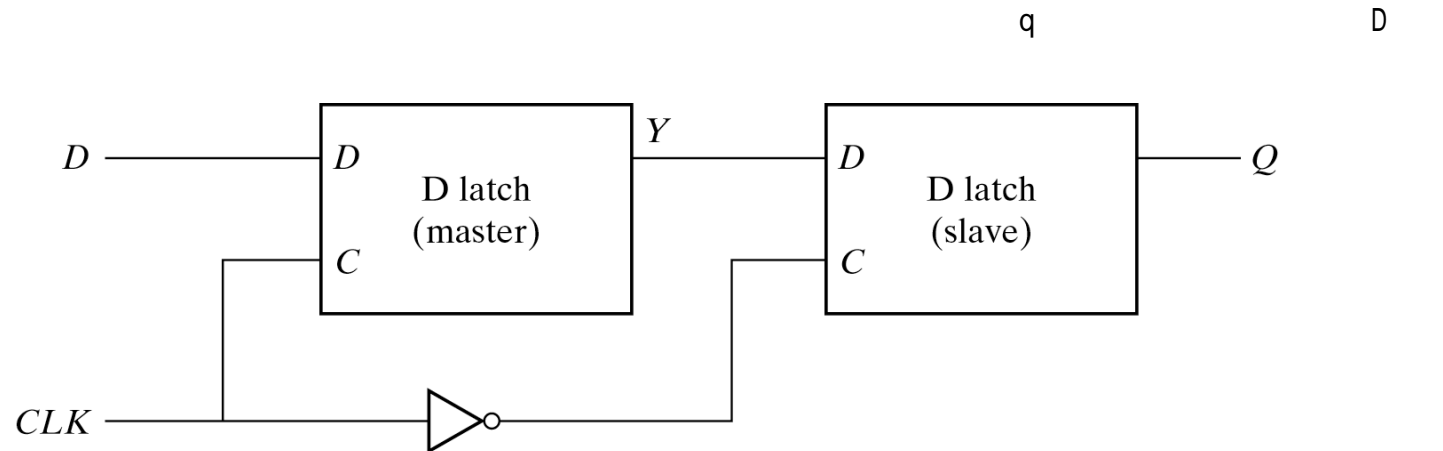


Fig. 5-9 Master-Slave *D* Flip-Flop

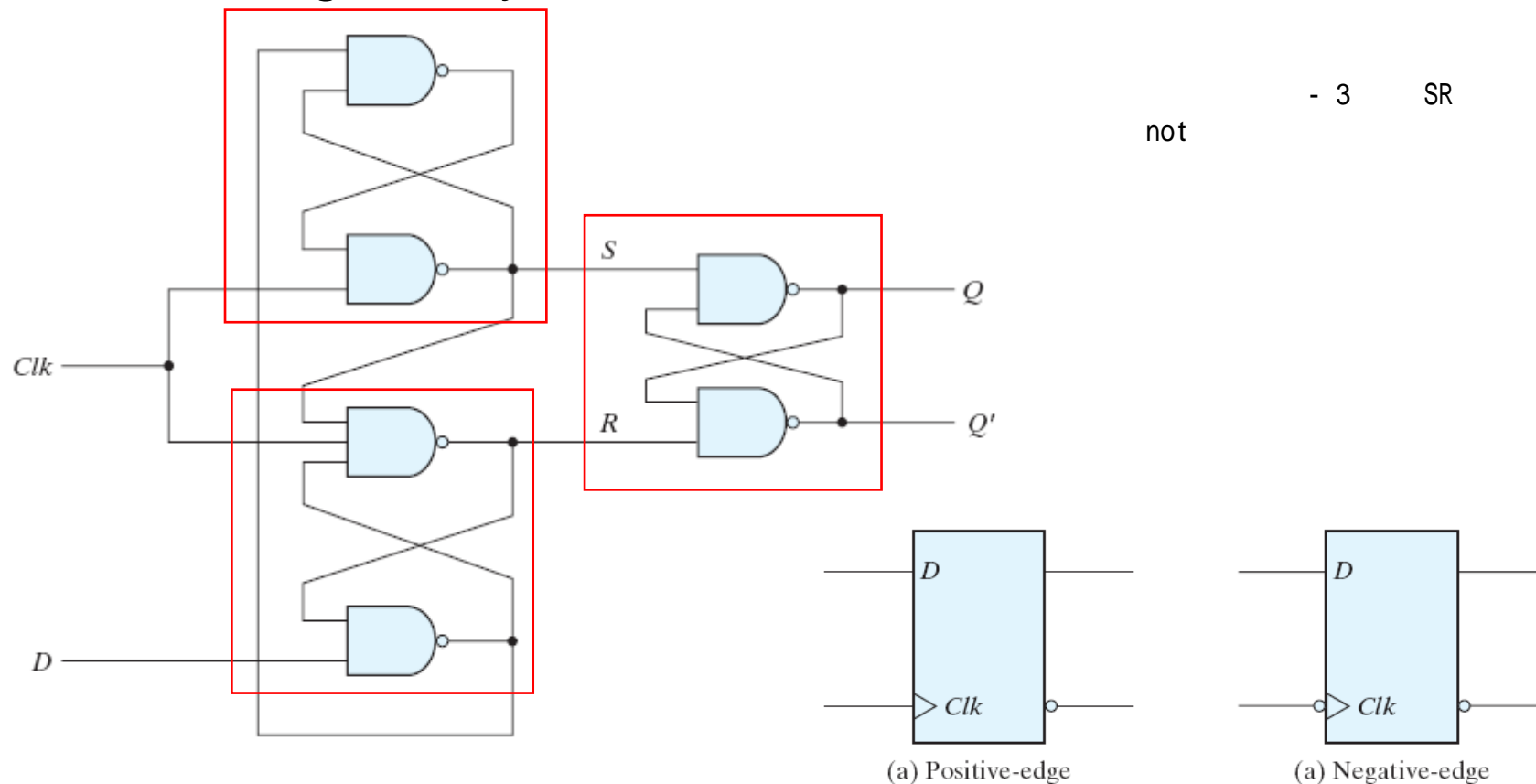5.4 Flip-flops - Edge-Triggered Flip-Flop


- D-type positive edge triggered flip flop
 - Consist of 3 SR-latches
 - Q changes only when C becomes 0 to 1



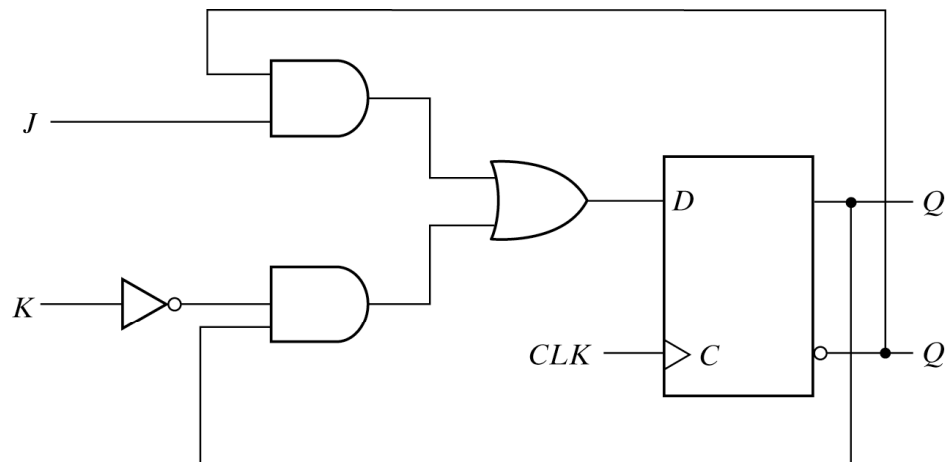
5.4 Flip-flops - Other Flip-Flop

- JK flip-flop $\begin{matrix} J=1, K=0 & Q=1 \\ J=K=0 & , J=0, K=1 & Q=0 \end{matrix}$ (flip-flop complement)

- Performs three operations
- Set(J), Reset(K), Complement(J=K=1)
- $D = JQ' + K'Q$



(a) Circuit diagram

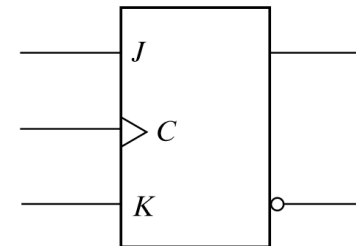

(b) Graphic symbol

Fig. 5-12 JK Flip-Flop

5.4 Flip-flops - Other Flip-Flop

● T flip-flop

- Complementing flip-flop

- $D = TQ' + T'Q$

JK


J K

- JK


0/1, 1/0

T 1


flip-flop, 0

 

(a) From JK flip-flop

 

(b) From D flip-flop

 

(c) Graphic symbol

Fig. 5-13 T Flip-Flop

5.4 Flip-flops - Characteristic tables

● Flip-flop characteristic tables

$$Q(t+1) = JQ' + K'Q$$

JK Flip-Flop			
<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q'(t)</i>	Complement

SR Flip-Flop			
<i>S</i>	<i>R</i>	<i>Q(t+1)</i>	Operation
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

D Flip-Flop		
<i>D</i>	<i>Q(t + 1)</i>	
0	0	Reset
1	1	Set

T Flip-Flop		
<i>T</i>	<i>Q(t + 1)</i>	
0	<i>Q(t)</i>	No change
1	<i>Q'(t)</i>	Complement

$$Q(t+1) = D$$

$$Q(t+1) = TQ' + T'Q$$

5. Flip-flops - Excitation table

Excitation Table

Table 5.12
Flip-Flop Excitation Tables

$Q(t)$	$Q(t = 1)$	J	K	$Q(t)$	$Q(t = 1)$	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

(a) JK

(b) T

SR Flip-Flop


$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

D Flip-Flop

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

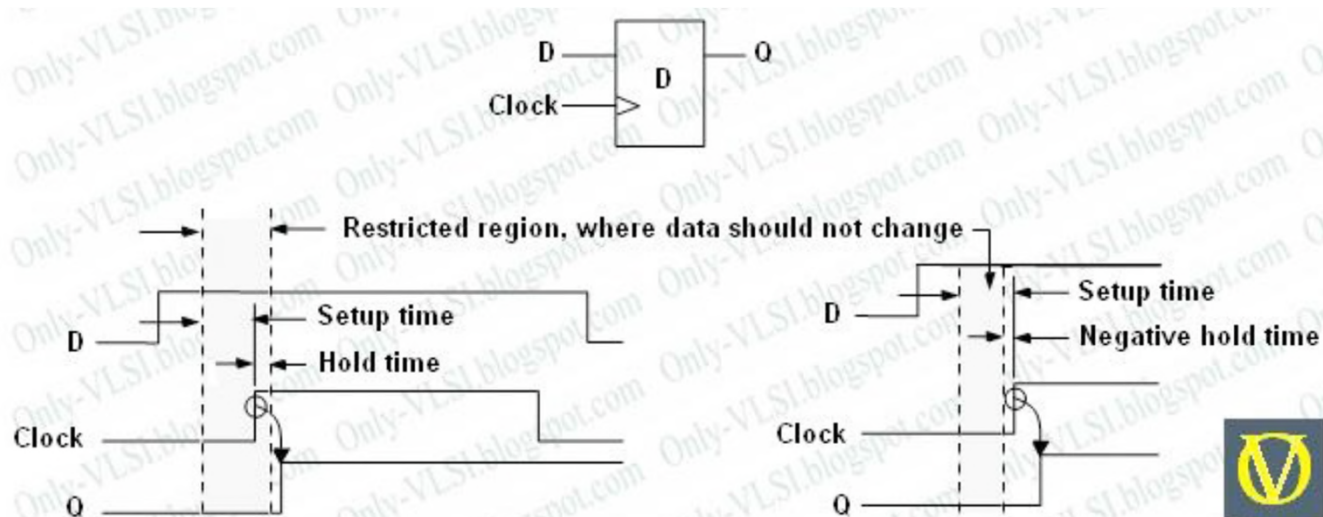5.4 Flip-flops - Terminologies

- *Setup time*: Time in which D input must be maintained at a constant value prior to applying the clock.
- *Hold time*: Time when D input must not change after the application of the positive transition of the pulse.
- *Propagation delay time*: Time interval between the trigger edge and the stabilization of the output to the new state.




(Source: only-vlsi.blogspot.com)

5.5 Analysis of clocked sequential circuits

- Behavior of clocked sequential circuit is determined from input, output and present state
- Output, next state are a function of input and present state

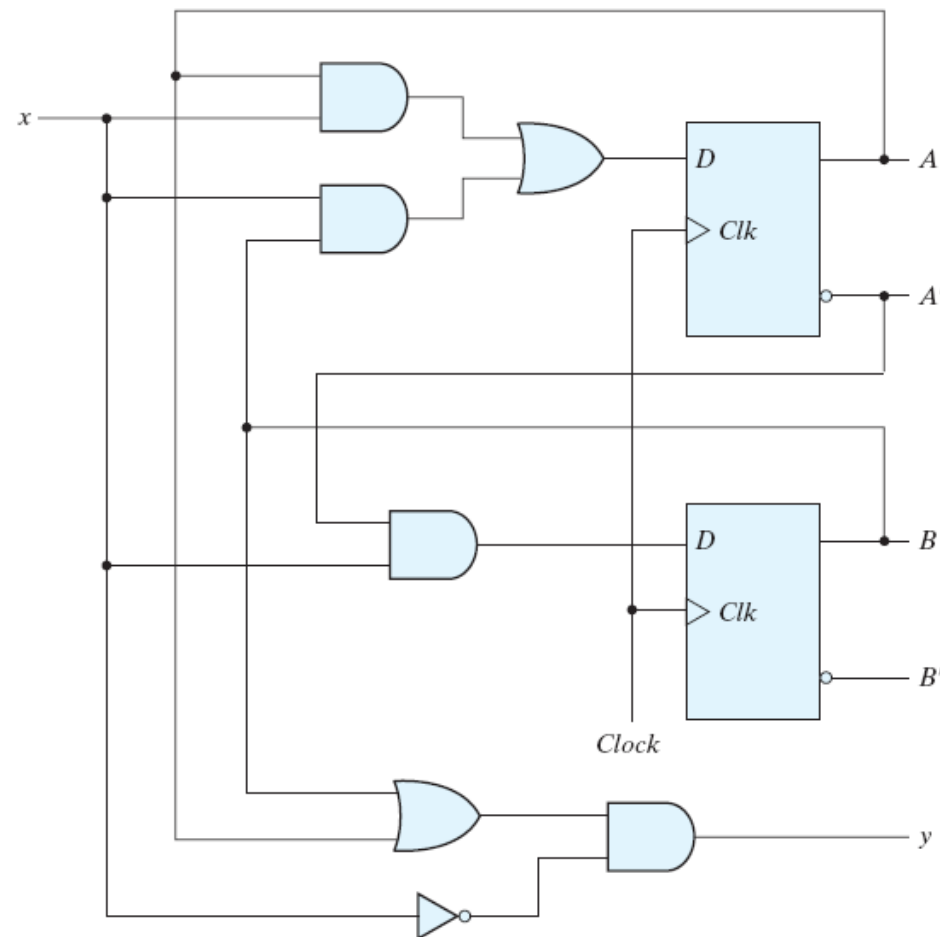5.5 Analysis of clocked sequential circuits - State equations

- Specifies the next state and output as a function of the present state and inputs
- $A(t+1) = Ax + Bx$
- $B(t+1) = A'x$
- $Y = (A+B)x'$



5.5 Analysis of clocked sequential circuits - State table

- Time sequence table of inputs, outputs and flip-flop states
- two types of state table exist

Table 5-2
State Table for the Circuit of Fig. 5-15

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Table 5-3
Second Form of the State Table

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

5.5 Analysis of clocked sequential circuits - State diagram

- A kind of flow diagram
- Can be derived from state table
- State-circle, transition-line, I/O

Table 5-2
State Table for the Circuit of Fig. 5-15

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

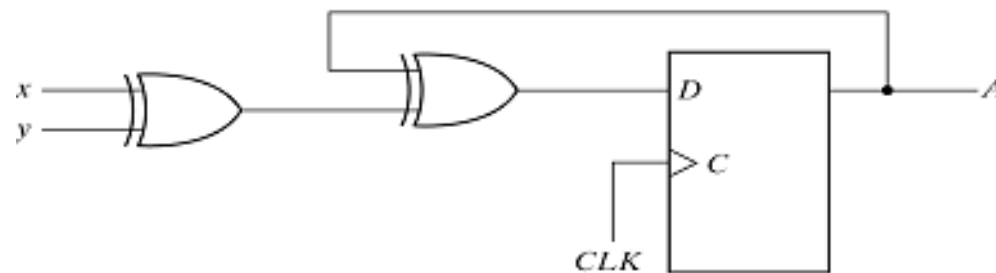5.5 Analysis of clocked sequential circuits - Analysis with D flip-flops

- Input equation : $D_A = A \oplus x \oplus y$
- State equation is equal to input equation



(a) Circuit diagram



(c) State diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

Fig. 5-17 Sequential Circuit with D Flip-Flop


5.5 Analysis of clocked sequential circuits - Analysis with JK flip-flops

- State equation is not the same as the input equation
- Have to refer characteristic table or characteristic equation

- Input equations

$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax'$$

 

5.5 Analysis of clocked sequential circuits - Analysis with JK flip-flops

State table and state diagram

Table 5-4
State Table for Sequential Circuit with JK Flip-Flops

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

5.5 Analysis of clocked sequential circuits - Analysis with T flip-flops

- Input equations and output equation


$$T_A = Bx, \quad T_B = x$$

$$y = AB$$

- State equations are derived from characteristic equation

$$A(t+1) = T_A A' + T_A' A$$

$$B(t+1) = T_B B' + T_B' B$$

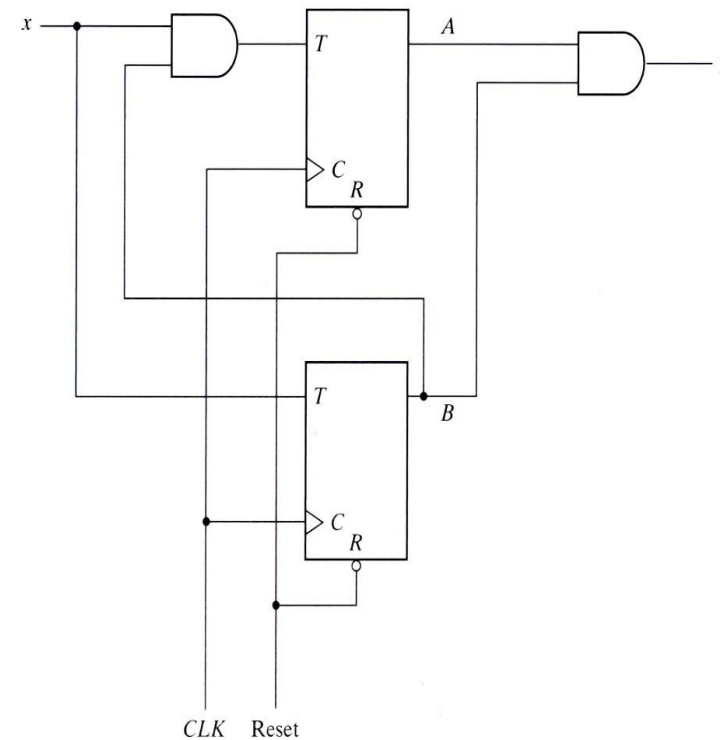


(a) Circuit diagram

5.5 Analysis of clocked sequential circuits - Analysis with T flip-flops

Table 5-5
State Table for Sequential Circuit with T Flip-Flops

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

5.7 State reduction and assignment

- State reduction is used to reduce the number of flip-flop
- Only input/output sequences are important
- Interested in present states that go to the same next state and have the same output

5.7 State reduction and assignment - State reduction

Table 5-6
State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

 


Fig. 5-22 State Diagram

5.7 State reduction and assignment - State reduction

Table 5-8
Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 


Fig. 5-23 Reduced State Diagram

5.7 State reduction and assignment - State assignment

- m states circuit, codes must contain n bits where $2^n \geq m$
- Three possible binary state assignments

Table 5-9
Three Possible Binary State Assignments

State	Assignment 1 Binary	Assignment 2 Gray code	Assignment 3 One-hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

5.8 Design procedure

- Sequential circuit design : requires state table
⇒ Combinational circuit : truth table
- The number of flip-flop is determined from the number of states in circuit
- If 2^n states exist, there are n flip-flops

5.8 Design procedure

- Design steps

- 1) Derive a state diagram or state table
- 2) Reduce the number of states if necessary
- 3) Assign binary code to the state
- 4) Choose the type of flip-flops to be used
- 5) Derive the flip-flop input equations and output equations
- 6) Draw the logic diagram

5.8 Design procedure

- Derive a state diagram
 - Sequential detector
 - Three or more consecutive 1's in a string of bits coming through an input line

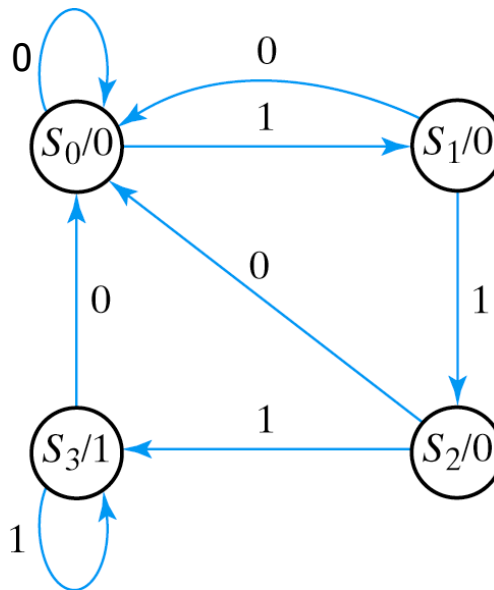


Fig. 5-24 State Diagram for Sequence Detector

5.8 Design procedure - Synthesis using D flip-flops

- Input equations are obtained directly from the next states

Table 5-11
State Table for Sequence Detector

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	1

5.8 Design procedure - Synthesis using D flip-flops

● K-maps and logic diagram

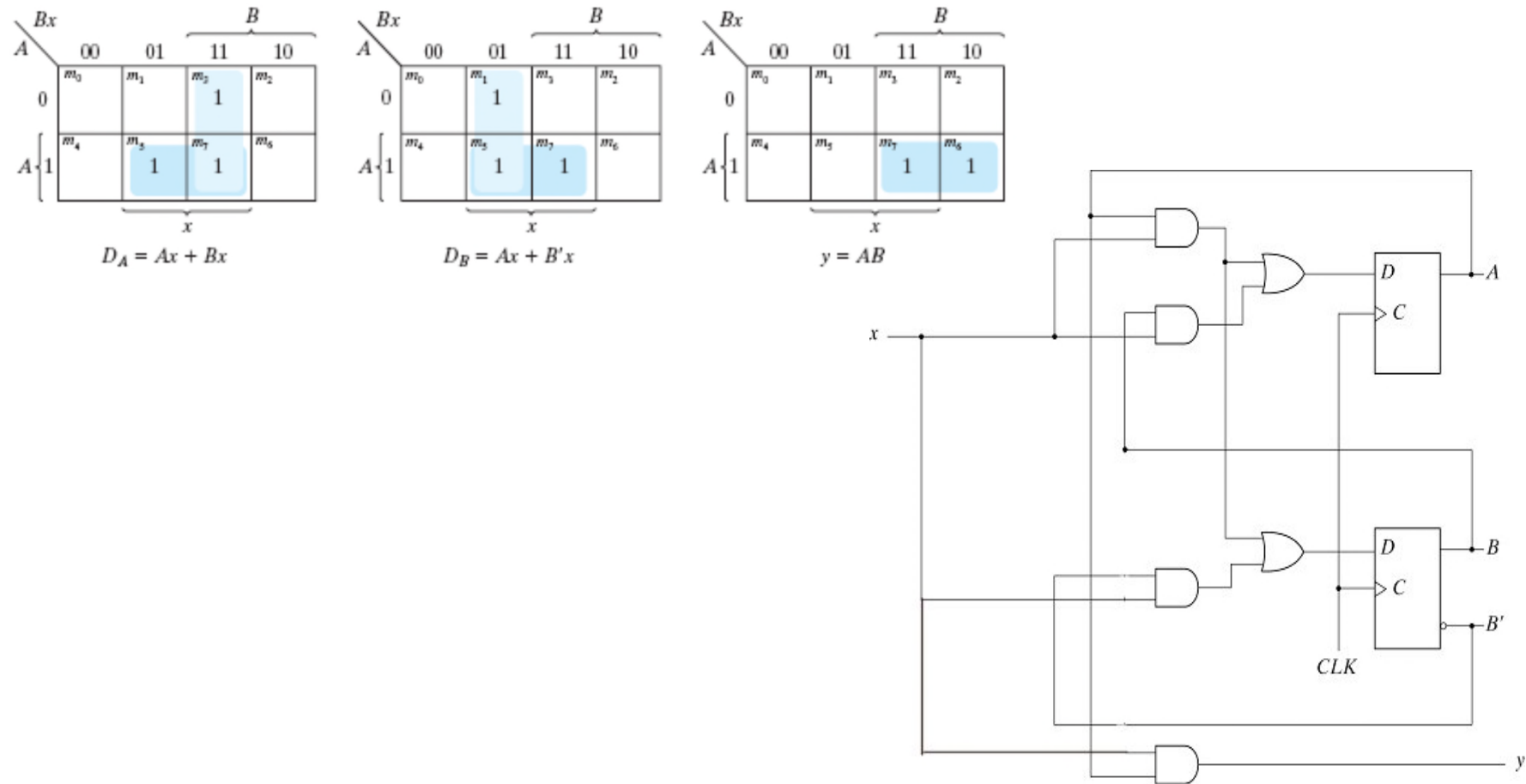


Fig. 5-26 Logic Diagram of Sequence Detector

5.8 Design procedure - Synthesis with JK flip-flops

- Input equations evaluated from the present state to next state transition

Table 5-13
State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

5.8 Design procedure - Synthesis with JK flip-flops

● K-maps and logic diagram

	Bx		B	
	00	01	11	10
A				
0				1
1	X	X	X	X

x

$$J_A = Bx'$$

	Bx		B	
	00	01	11	10
A				
0	X	X	X	X
1			1	

x

$$K_A = Bx$$

	Bx		B	
	00	01	11	10
A				
0		1	X	X
1		1	X	X

x

$$J_B = x$$

	Bx		B	
	00	01	11	10
A				
0	X	X		1
1	X	X	1	

x

$$K_B = (A \oplus x)'$$

 


Fig. 5-27 Maps for J and K Input Equations

5.8 Design procedure - Synthesis using T flip-flops

- 3-bit binary counter
- 3-bit counter has 3 flip-flops and can count from 0 to $2^n - 1$ ($n=3$)

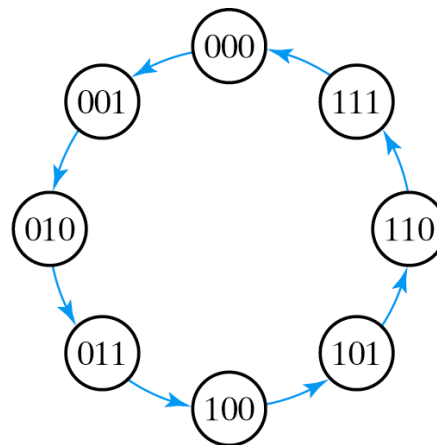



Fig. 5-29 State Diagram of 3-Bit Binary Counter

5.8 Design procedure - Synthesis using T flip-flops


State table and logic diagram

Table 5-14
State Table for 3-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

 
 
$$T_{A2}=A_1A_0, \quad T_{A1}=A_0, \quad T_{A0}=1$$




5.6 HDL for sequential circuits

- Two kinds of behavioral statements
- Initial : executes only once
- Always : executes repeatedly until the simulation terminates

5.6 HDL for sequential circuits - Flip-flops and latches

● D-latch

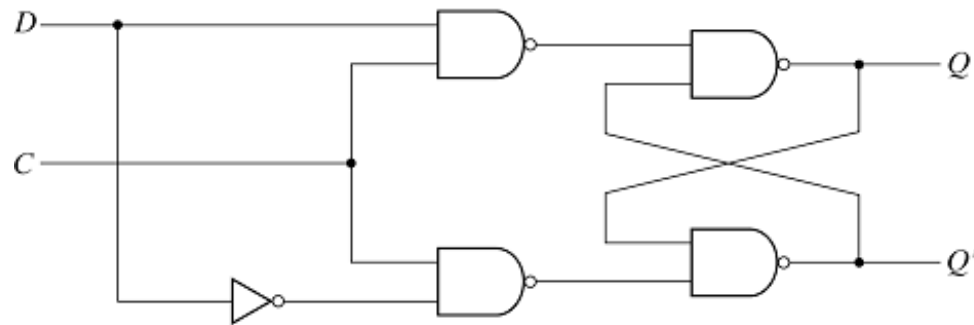

HDL Example 5-1

```
//Description of D latch (See Fig. 5-6)
module D_latch (Q,D,control);
    output Q;
    input D,control;
    reg Q;
    always @ (control or D)
        if (control) Q = D;      //Same as: if (control == 1)
endmodule
```

5.6 HDL for sequential circuits - Flip-flops and latches

● D flip-flop

- D flip-flop with asynchronous reset



```
//D flip-flop
module D_FF (Q,D,CLK);
    output Q;
    input D,CLK;
    reg Q;
    always @ (posedge CLK)
        Q = D;
endmodule

//D flip-flop with asynchronous reset.
module DFF (Q,D,CLK,RST);
    output Q;
    input D,CLK,RST;
    reg Q;
    always @(posedge CLK or negedge RST)
        if (~RST) Q = 1'b0;    // Same as: if (RST == 0)
        else Q = D;
endmodule
```

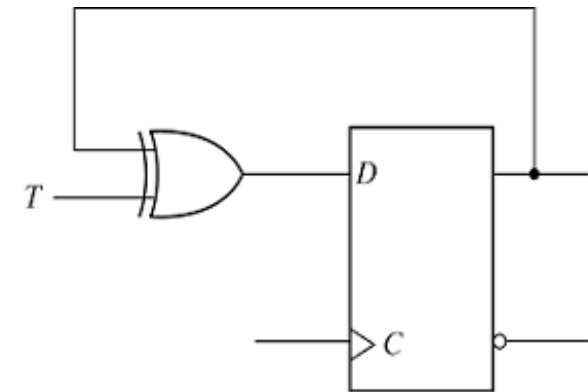
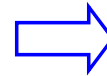
5.6 HDL for sequential circuits - Flip-flops and latches

● T flip-flop from D flip-flop

```
//T flip-flop from D flip-flop and gates
module TFF (Q,T,CLK,RST);
    output Q;
    input T,CLK,RST;
    wire DT;
    assign DT = Q ^ T ;
    //Instantiate the D flip-flop
    DFF TF1 (Q,DT,CLK,RST);
endmodule
```




```
//JK flip-flop from D flip-flop and gates
module JKFF (Q,J,K,CLK,RST);
    output Q;
    input J,K,CLK,RST;
    wire JK;
    assign JK = (J & ~Q) | (~K & Q);
    //Instantiate D flipflop
    DFF JK1 (Q,JK,CLK,RST);
endmodule
```

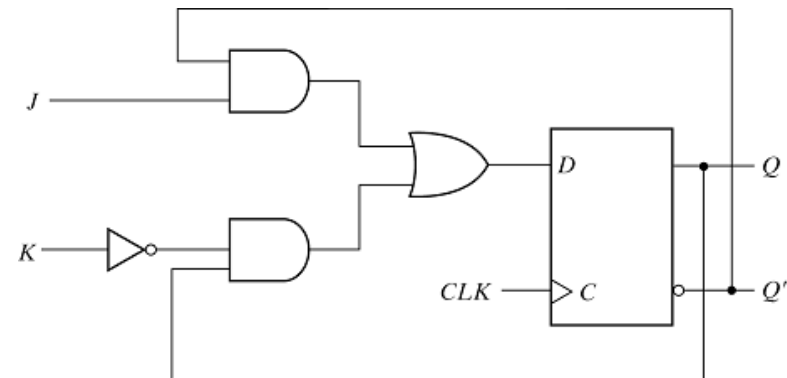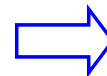

5.6 HDL for sequential circuits - Flip-flops and latches

● JK flip-flop

 

HDL Example 5-4

```
// Functional description of JK flip-flop
module JK_FF (J,K,CLK,Q,Qnot);
    output Q,Qnot;
    input J,K,CLK;
    reg Q;
    assign Qnot = ~ Q ;
    always @ (posedge CLK)
        case ({J,K})
            2'b00: Q = Q;
            2'b01: Q = 1'b0;
            2'b10: Q = 1'b1;
            2'b11: Q = ~ Q;
        endcase
endmodule
```

5.6 HDL for sequential circuits - State diagram

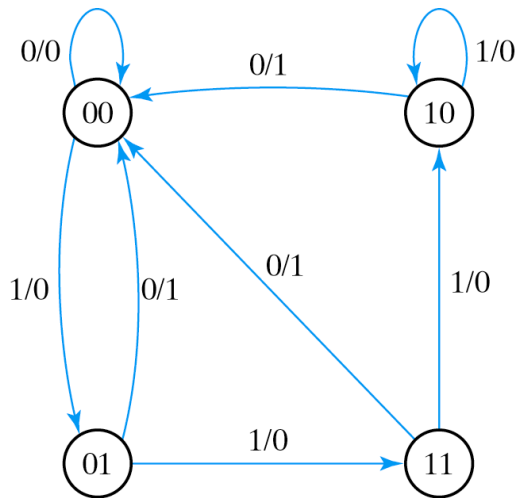


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

(Mealy state diagram)

```

module Mealy_md1 (x,y,CLK,RST);
  input x,CLK,RST;
  output y;
  reg y;
  reg [1:0] Prstate, Nxtstate;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST)
    if (~RST) Prstate = S0; //Initialize to state S0
    else Prstate = Nxtstate; //Clock operations
  always @ (Prstate or x) //Determine next state
    case (Prstate)
      S0: if (x) Nxtstate = S1;
          else Nxtstate = S0;
      S1: if (x) Nxtstate = S3;
          else Nxtstate = S0;
      S2: if (~x) Nxtstate = S0;
          else Nxtstate = S2;
      S3: if (x) Nxtstate = S2;
          else Nxtstate = S0;
    endcase
  always @ (Prstate or x) //Evaluate output
    case (Prstate)
      S0: y = 0;
      S1: if (x) y = 1'b0; else y = 1'b1;
      S2: if (x) y = 1'b0; else y = 1'b1;
      S3: if (x) y = 1'b0; else y = 1'b1;
    endcase
endmodule
  
```

5.6 HDL for sequential circuits - State diagram


 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

(Moore state diagram)

```
//Moore state diagram (Fig. 5-19)
module Moore_mdl (x,AB,CLK,RST);
  input x,CLK,RST;
  output [1:0]AB;
  reg [1:0] state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST)
    if (~RST) state = S0; //Initialize to state S0
    else
      case (state)
        S0: if (~x) state = S1; else state = S0;
        S1: if (x) state = S2; else state = S3;
        S2: if (~x) state = S3; else state = S2;
        S3: if (~x) state = S0; else state = S3;
      endcase
  assign AB = state; //Output of flip-flops
endmodule
```

 5.6 HDL for sequential circuits - Structural description



(a) Circuit diagram

```
module Tcircuit (x,y,A,B,CLK,RST);
    input x,CLK,RST;
    output y,A,B;
    wire TA,TB;
    //Flip-flip input equations
    assign TB = x,
           TA = x & B;
    //Output equation
    assign y = A & B;
    //Instantiate T flip-flops
    T_FF BF (B,TB,CLK,RST);
    T_FF AF (A,TA,CLK,RST);
endmodule
```

```

module T_FF (Q,T,CLK,RST);
    output Q;
    input T,CLK,RST;
    reg Q;
    always @ (posedge CLK or negedge RST)
        if (~RST) Q = 1'b0;
        else Q = Q ^ T;
endmodule

```

5.6 HDL for sequential circuits - Structural description

```

module testTcircuit;
  reg x,CLK,RST;  //inputs for circuit
  wire y,A,B;    //output from circuit
  Tcircuit TC (x,y,A,B,CLK,RST);  // instantiate circuit
  initial
    begin
      RST = 0;
      CLK = 0;
      #5 RST = 1;
      repeat (16)
        #5 CLK = ~CLK;
    end
  initial
    begin
      x = 0;
      #15 x = 1;
      repeat (8)
        #10 x = ~ x;
    end
endmodule

```

(Stimulus and output)

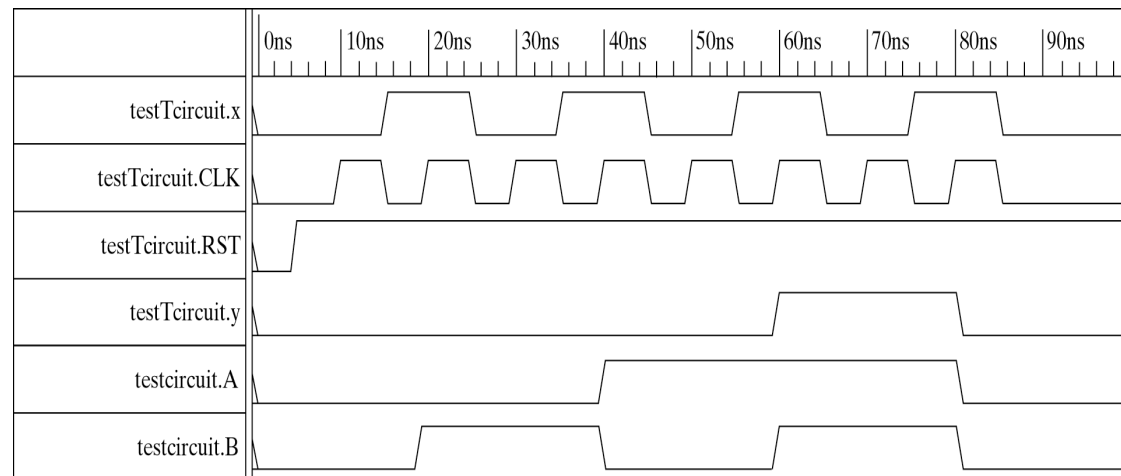


Fig. 5-21 Simulation Output of HDL Example 5-7

5.6 HDL for sequential circuits

```
module Mealy_Zero_Detector (  
    output reg y_out,  
    input      x_in, clock, reset  
);  
    reg [1: 0]    state, next_state;  
    parameter     S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
  
    always @ (posedge clock, negedge reset)    // state transition  
    if (reset == 0) state <= S0;  
    else state <= next_state;  
  
    always @ (state, x_in) // Form the next state  
    case (state)  
        S0:    if (x_in) next_state = S1; else next_state = S0;  
        S1:    if (x_in) next_state = S3; else next_state = S0;  
        S2:    if (~x_in) next_state = S0; else next_state = S2;  
        S3:    if (x_in) next_state = S2; else next_state = S0;  
    endcase  
  
    always @ (state, x_in) // Form the output  
    case (state)  
        S0:    y_out = 0;  
        S1, S2, S3: y_out = ~x_in;  
    endcase  
endmodule  
  
module t_Mealy_Zero_Detector;  
    wire t_y_out;  
    reg t_x_in, t_clock, t_reset;  
  
    Mealy_Zero_Detector M0 (t_y_out, t_x_in, t_clock, t_reset);  
  
    initial #200 $finish;  
    initial begin t_clock = 0; forever #5 t_clock = ~t_clock; end
```

```
    initial fork  
        t_reset = 0;  
        #2 t_reset = 1;  
        #87 t_reset = 0;  
        #89 t_reset = 1;  
        #10 t_x_in = 1;  
        #30 t_x_in = 0;  
        #40 t_x_in = 1;  
        #50 t_x_in = 0;  
        #52 t_x_in = 1;  
        #54 t_x_in = 0;  
        #70 t_x_in = 1;  
        #80 t_x_in = 1;  
        #70 t_x_in = 0;  
        #90 t_x_in = 1;  
        #100 t_x_in = 0;  
        #120 t_x_in = 1;  
        #160 t_x_in = 0;  
        #170 t_x_in = 1;  
  
    join  
endmodule
```

5.6 HDL for sequential circuits

