

## Ch 4. Combinational logic

# 4.1 Introduction

## 4.2 Combinational circuits

- Outputs are determined from the present inputs
- Consist of input/output variables and logic gates

가 combinational circuit

 


Fig. 4-1 Block Diagram of Combinational Circuit

## 4.3 Analysis procedure

- To determine the function of circuit
- Analysis procedure
  - Make sure the circuit is combinational or sequential
  - Obtain the output Boolean functions or the truth table

## 4.3 Analysis procedure

- Boolean function
  - Label all gate outputs
  - Make output functions at each level
  - Substitute final outputs to input variables
- Truth table
  - Put the input variables to binary numbers
  - Determine the output value at each gate
  - Obtain truth table

## 4.3 Analysis procedure

**Table 4-1**  
Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	F <sub>2</sub>	F <sub>2</sub>	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	F <sub>1</sub>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

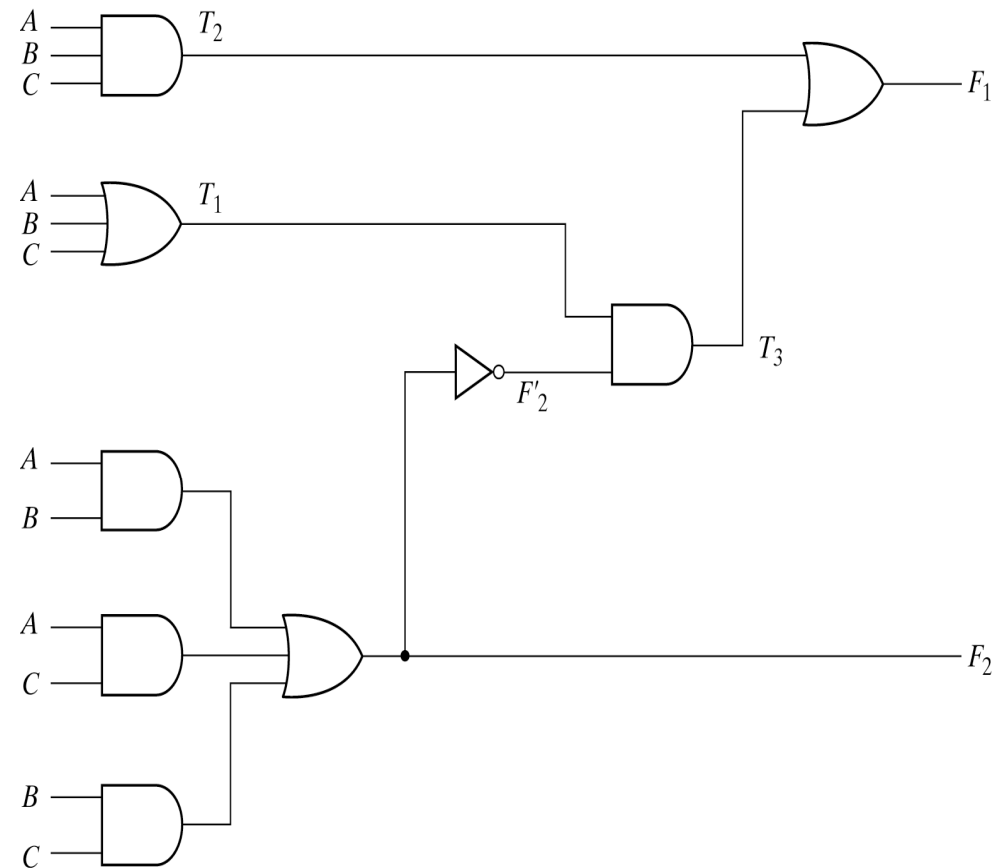


Fig. 4-2 Logic Diagram for Analysis Example

## 4.4 Design procedure

- Procedure to design
  - Determine the required number of input and output from specification
  - Assign a letter symbol to each input/output
  - Derive the truth table
  - Obtain the simplified Boolean functions
  - Draw the logic diagram and verify design correctness

## 4.4 Design procedure - Code conversion example

- BCD to excess-3 code converter
  - Excess-3 code : decimal digit+3
- Design procedure
  - 1) Determine inputs/outputs
    - Inputs : A,B,C,D (0000~1001)
    - Outputs : W,X,Y,Z (0011~1100)



## 4.4 Design procedure - Code conversion example

### 2) Derive truth table

**Table 4-2**  
*Truth Table for Code-Conversion Example*

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

## 4.4 Design procedure - Code conversion example

### 3) Obtain simplified Boolean functions

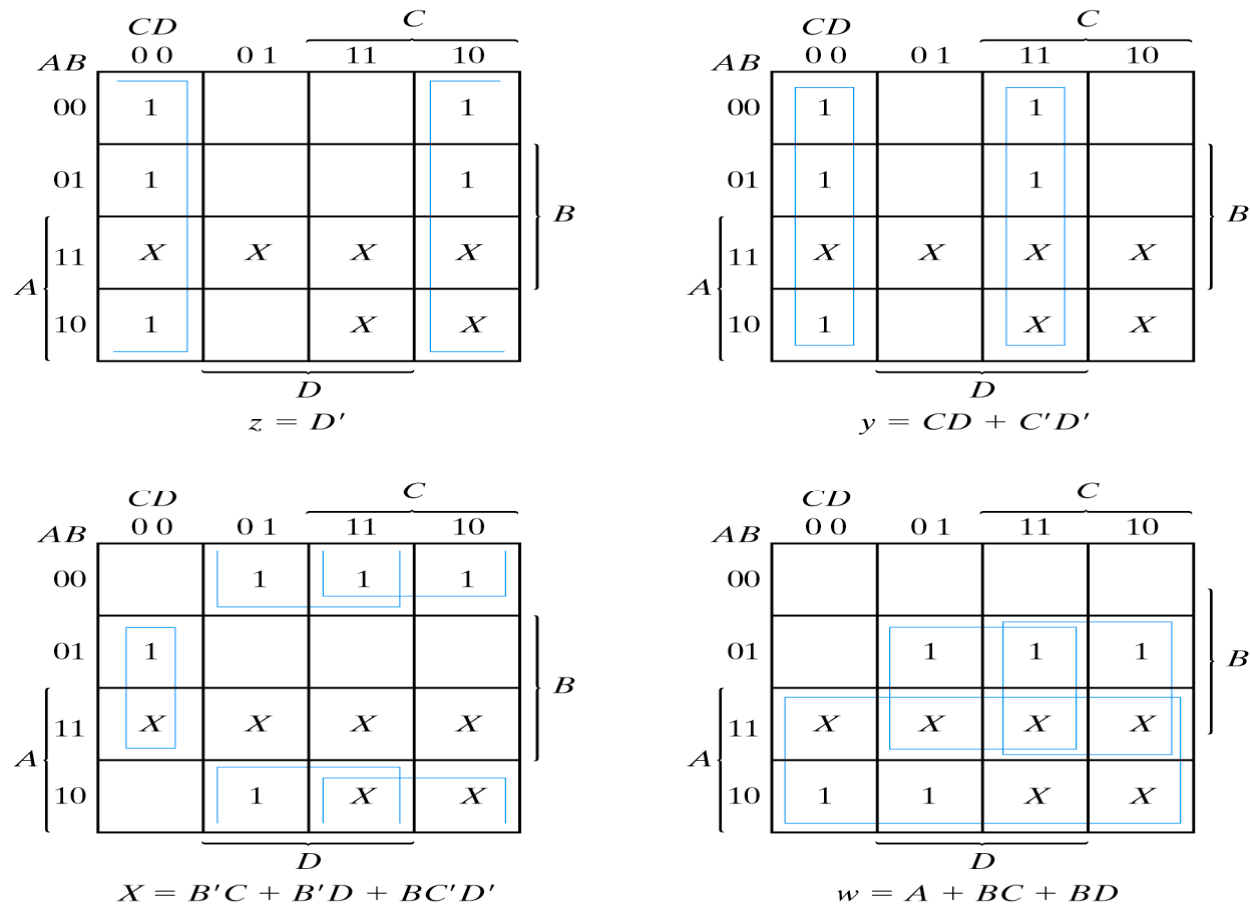


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

## 4.4 Design procedure - Code conversion example

### 4) Draw the logic diagram

$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$\begin{aligned} x &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)' \end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$

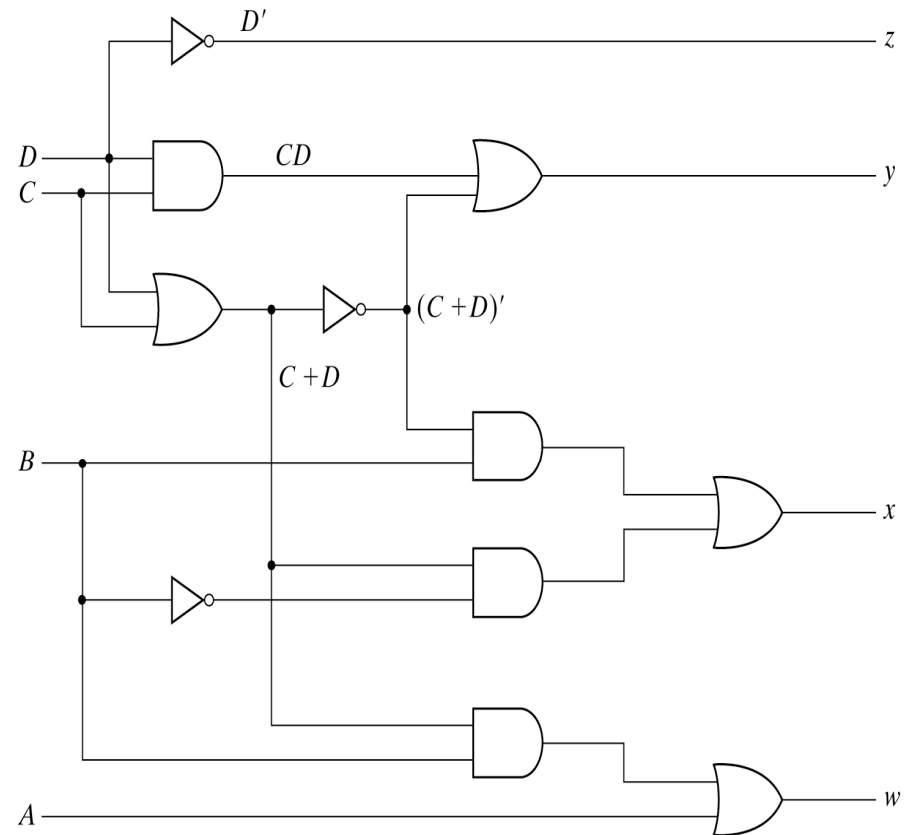


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

## 4.5 Binary adder-subtractor


- Binary adder
  - Half adder : performs the addition of 2-bits( $x+y$ )
  - Full adder : performs the addition of 3-bits( $x+y+z$ )
  - Two half adder can be employed to a full adder
- Realization of Binary adder-subtractor
  - Half adder
  - Full adder
  - Cascade of  $n$ -full adder
  - Providing a complementing circuit

## 4.5 Binary adder-subtractor - Half Adder

- Sum of 2 binary inputs
- Input : X(augend), Y(addend)  
Output : S(sum), C(carry)


**Table 4-3**  
*Half Adder*

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

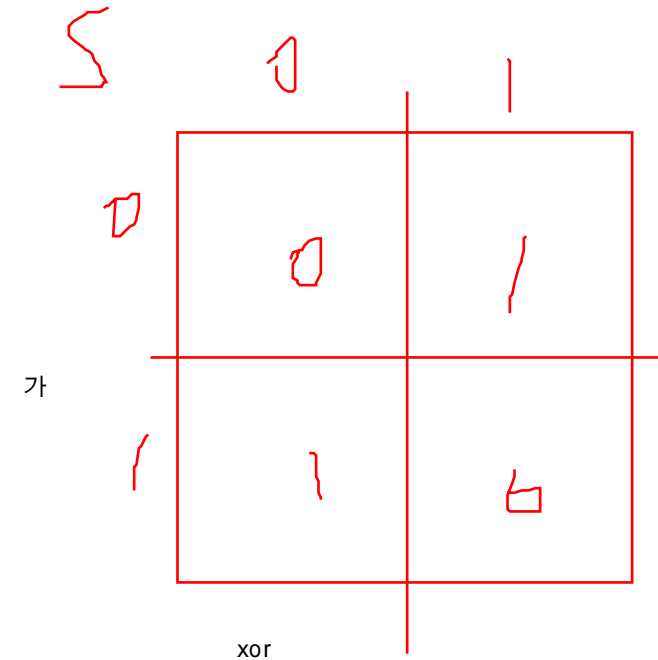


$$S = xy' + x'y$$


$$C = xy$$

 
 
## 4.5 Binary adder-subtractor - Half Adder


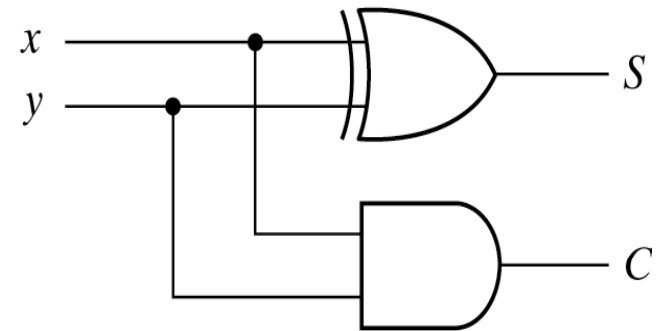
$$\begin{aligned} \text{(a) } S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$\begin{aligned} \text{(b) } S &= x \oplus y \\ C &= xy \end{aligned}$$

Fig. 4-5 Implementation of Half-Adder

## 4.5 Binary adder-subtractor - Full adder

- Sum of 3 binary inputs
- Input : X,Y(2 significant bits),Z(1 carry bit)
- Output : S(sum),C(carry)

**Table 4-4**  
*Full Adder*

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

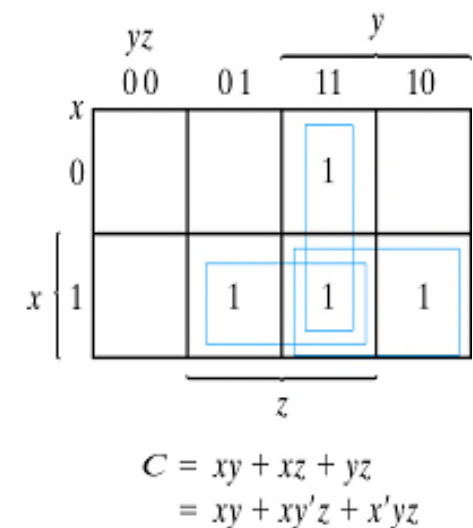
 


Fig. 4-6 Maps for Full Adder

## 4.5 Binary adder-subtractor - Full adder

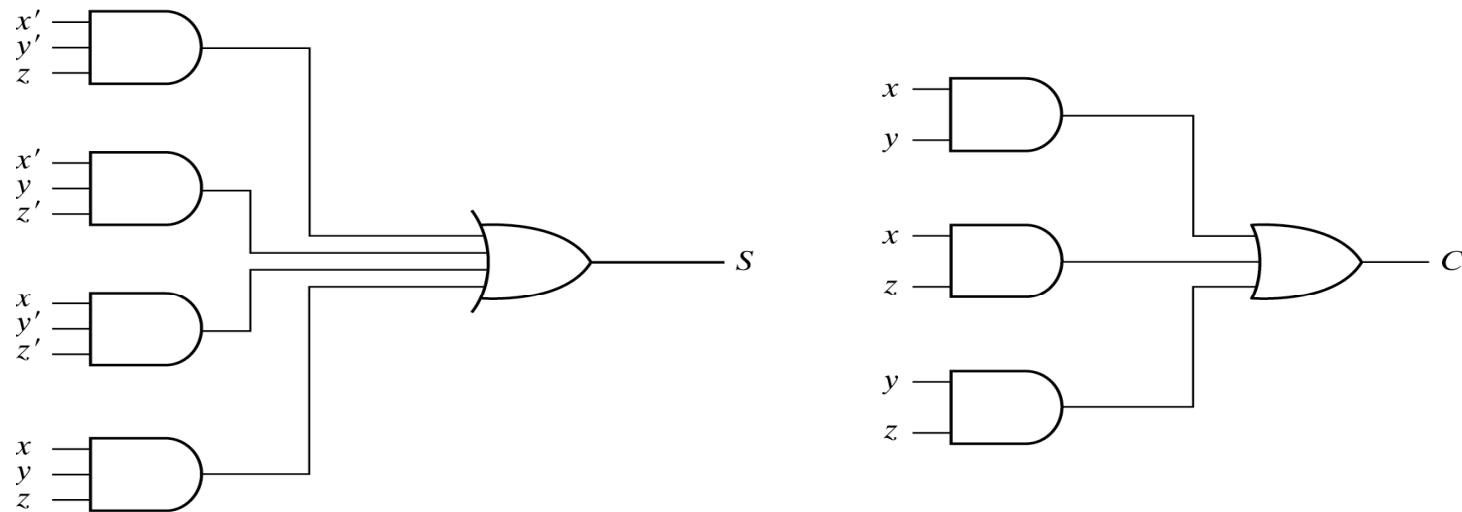


Fig. 4-7 Implementation of Full Adder in Sum of Products

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate



## 4.5 Binary adder-subtractor - Binary adder

### Sum of two n-bit binary numbers

#### – 4-bit adder

A=1011, B=0011

Subscript i:	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

(delay가 , 3 )

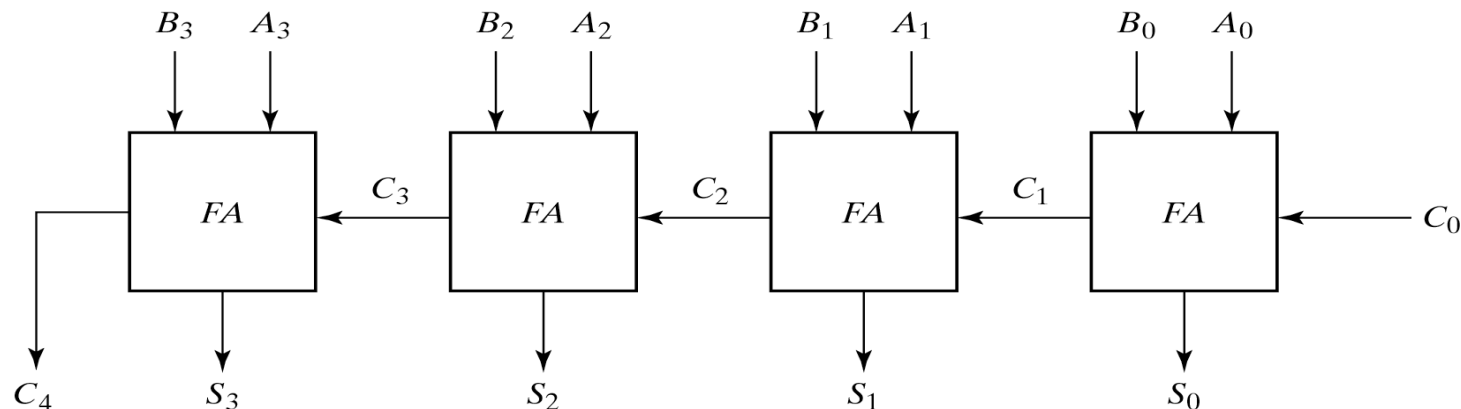


Fig. 4-9 4-Bit Adder

## 4.5 Binary adder-subtractor - Carry propagation

- Rising of delay time(carry delay)
- One solution is **carry lookahead**
- All carry is a function of  $P_i, G_i$  and  $C_0$

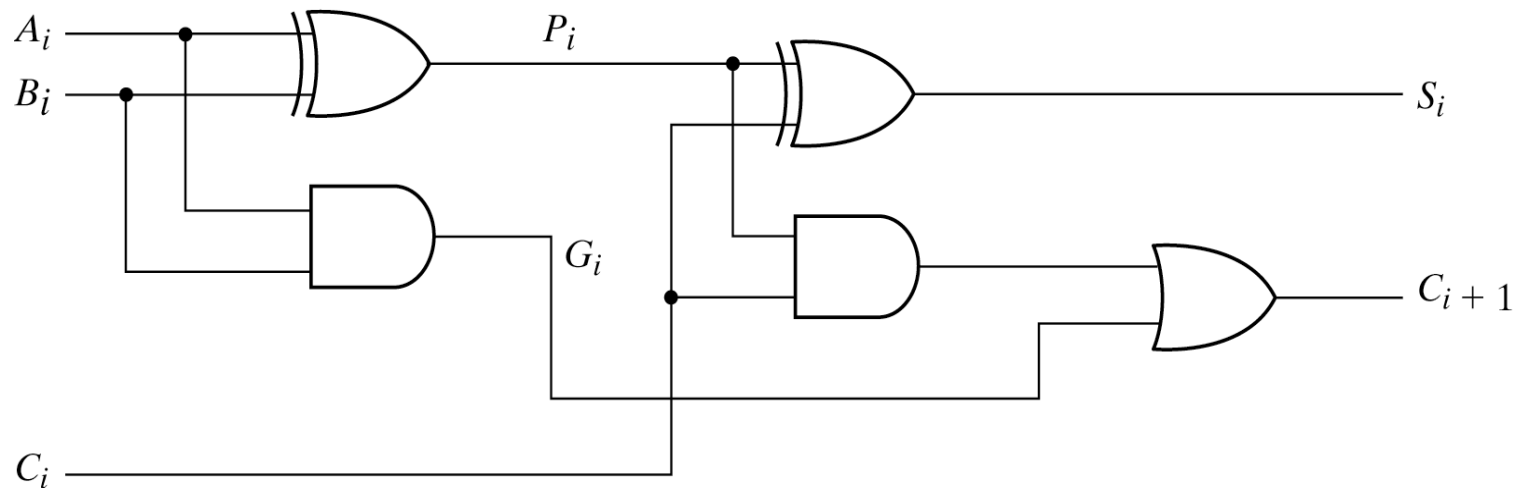


Fig. 4-10 Full Adder with P and G Shown

## 4.5 Binary adder-subtractor - Carry propagation

### ● Carry lookahead generator

$C_0$  = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

## 4.5 Binary adder-subtractor - Carry propagation

### 4-bit adder with carry lookahead

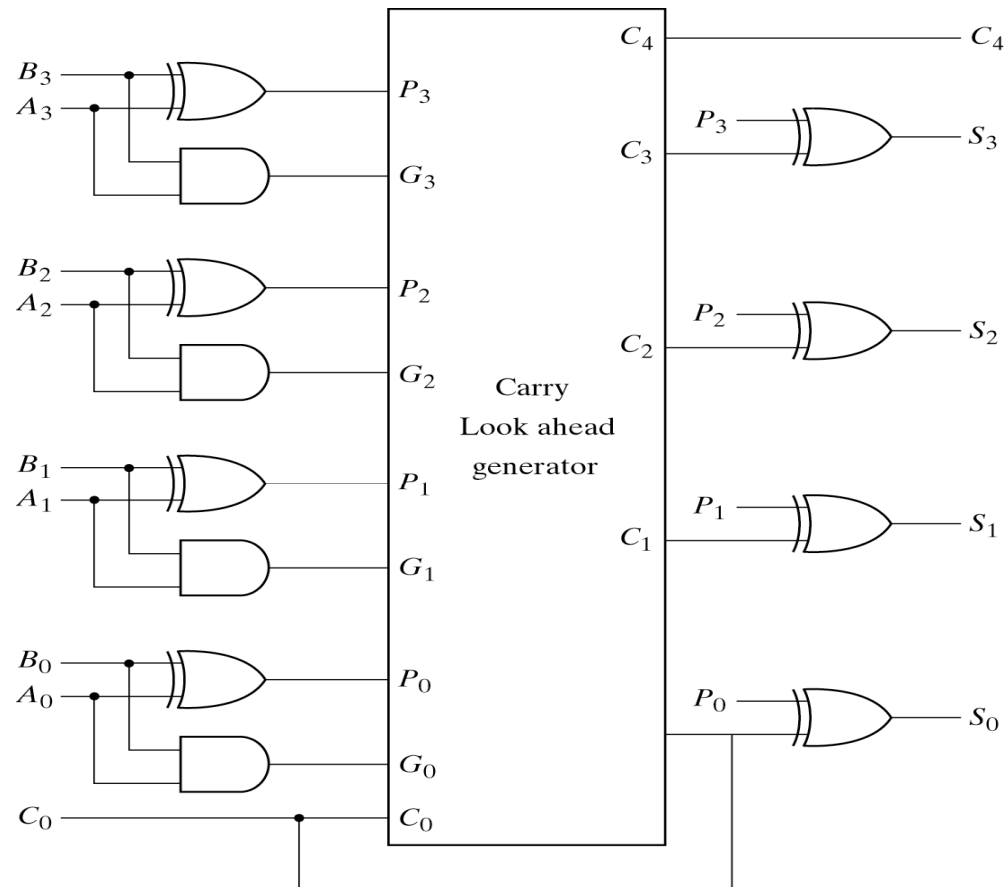


Fig. 4-12 4-Bit Adder with Carry Lookahead

## 4.5 Binary adder-subtractor - Binary subtractor

- $A - B$  equals  $A + (2\text{'s complement of } B)$
- When  $M=0$  (act as adder)  $M=1$  (subtractor)

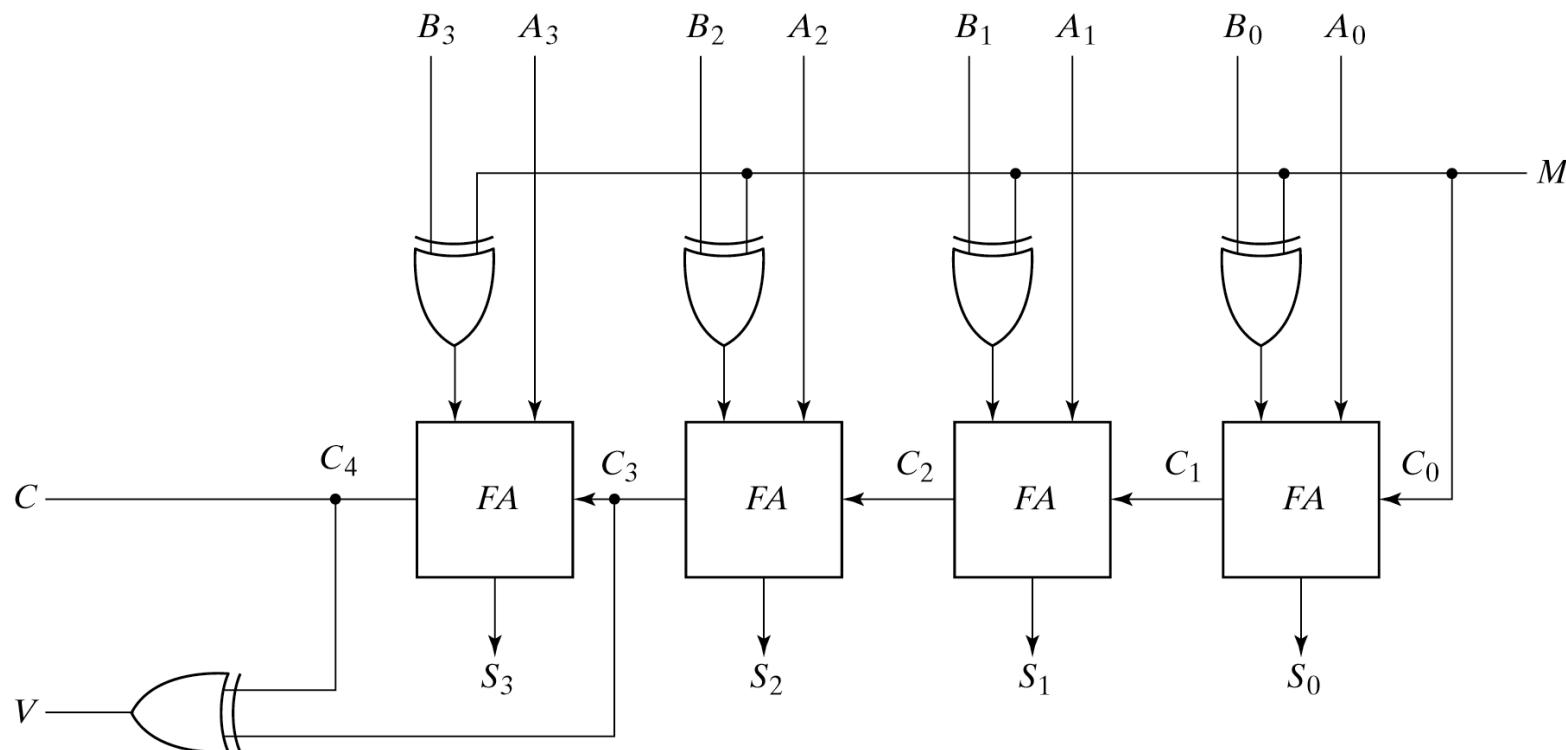


Fig. 4-13 4-Bit Adder Subtractor

## 4.5 Binary adder-subtractor - Overflow

- Sum of  $n$  digit number occupies  $n+1$  digit
- Occurs when two numbers are same sign

(examples of overflow)

carries:	0	1
+70	0	1000110
+80	0	1010000
<hr/>		
+150	1	0010110

carries:	1	0
-70	1	0111010
-80	1	0110000
<hr/>		
-150	0	1101010

## 4.6 Decimal adder

- Calculate binary and represent decimal in binary coded form
- Decimal adder for the BCD code

## 4.6 Decimal adder - BCD Adder

- BCD digit output of 2-BCD digit sum
- Carry arise if output 1010~1111
- $C = K + Z_8 Z_4 + Z_8 Z_2$


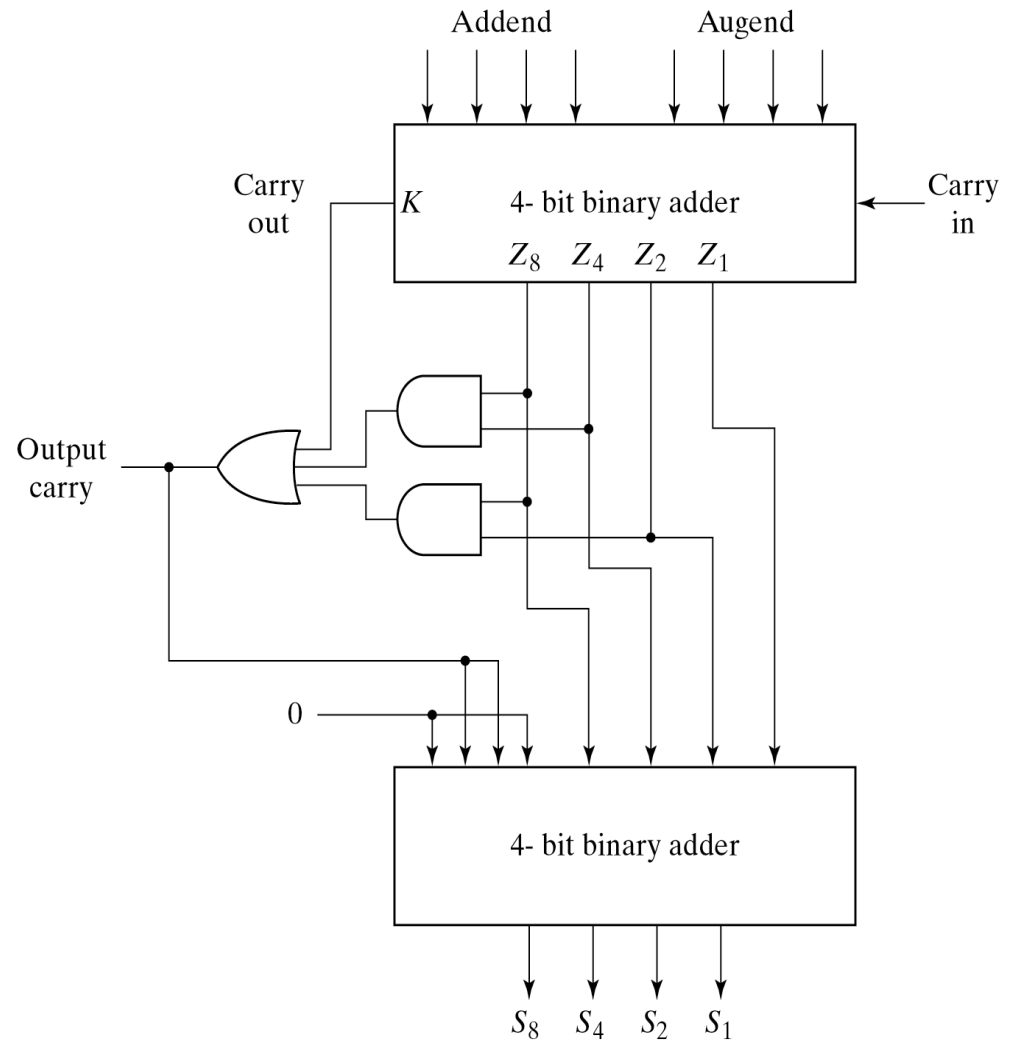


Fig. 4-14 Block Diagram of a BCD Adder

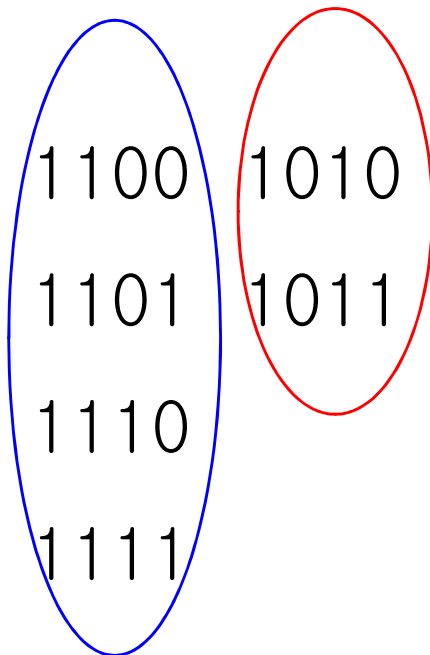

## 4.7 Binary multiplier

- 2bit x 2bit = 4bit(max)

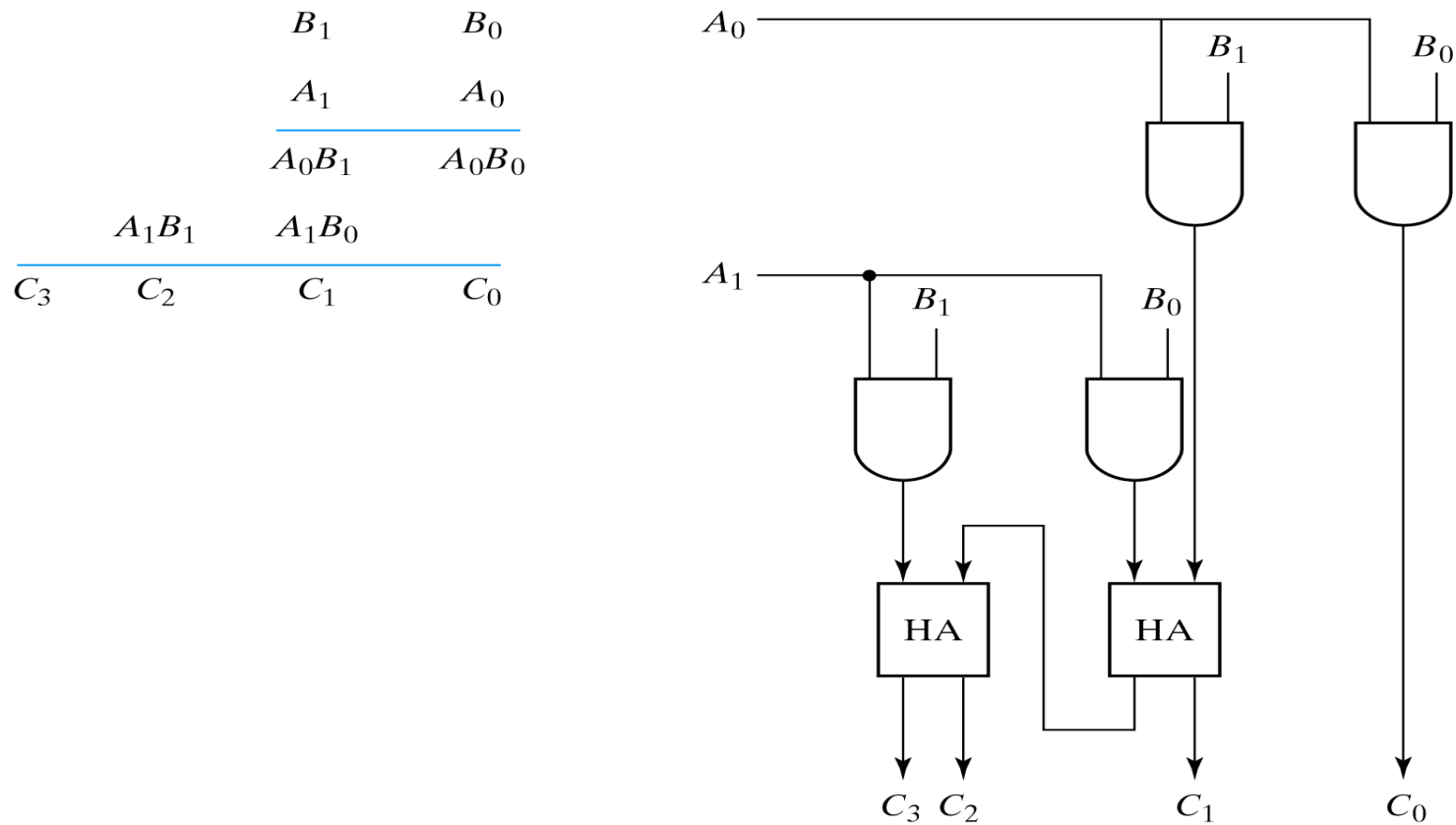


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

## 4.7 Binary multiplier

- (K-bit) x (J-bit)
  - (K x J) AND gates,  
(J-1) K-bit adder needed

$$\begin{array}{r} B_3 B_2 B_1 B_0 \\ \times \quad A_2 A_1 A_0 \\ \hline \end{array}$$

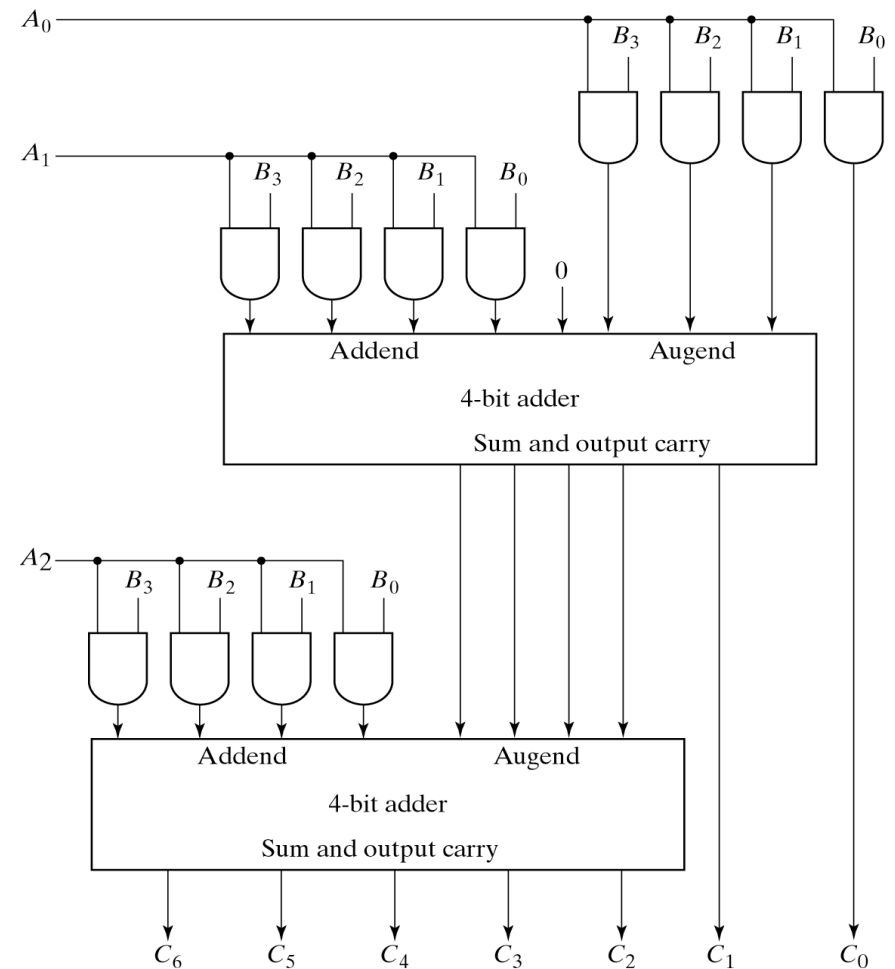


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

## 4.8 Magnitude comparator

- $X_i=1$  only if the pair of bits in  $i$  are equal
- $(A=B)=x_3x_2x_1x_0$
- $(A>B)=A_3B_3'+x_3A_2B_2'+x_3x_2A_1B_1'+x_3x_2x_1A_0B_0'$
- $(A<B)=A_3'B_3+x_3A_2'B_2+x_3x_2A_1'B_1+x_3x_2x_1A_0'B_0$

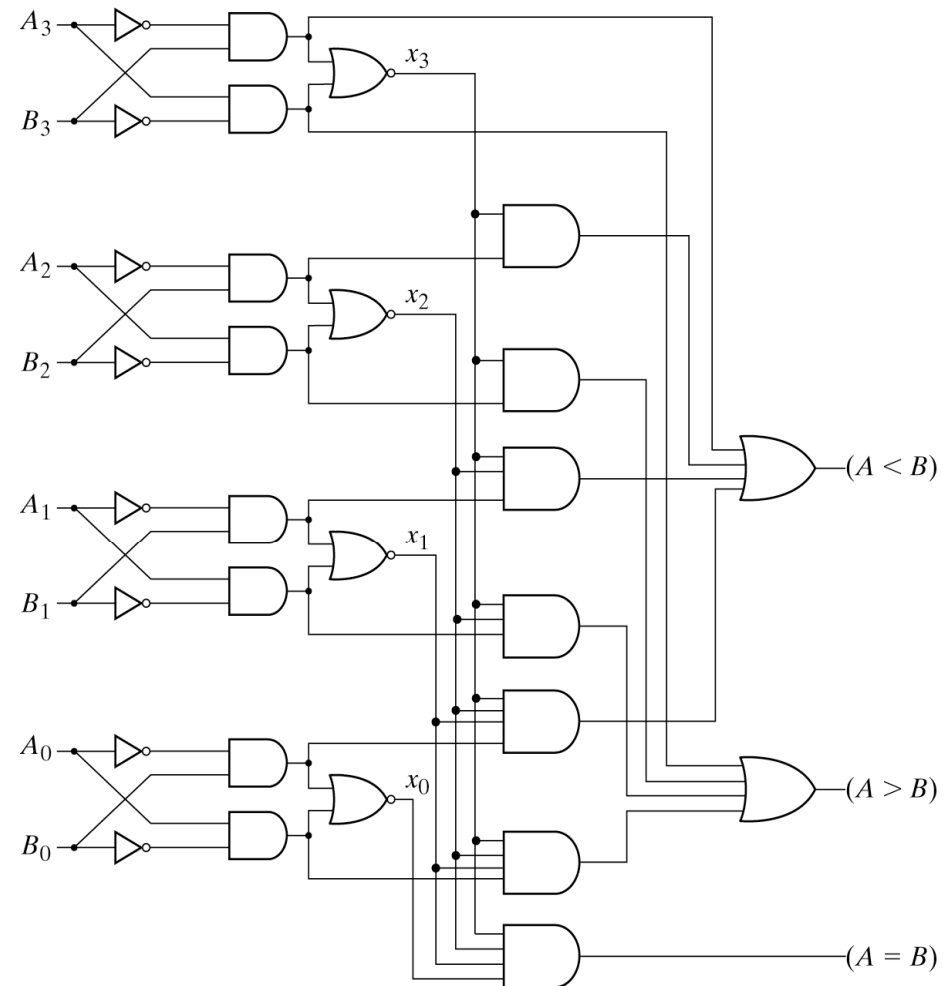


Fig. 4-17 4-Bit Magnitude Comparator

## 4.9 Decoders

- Generate the  $2^n$ (or less) minterms of  $n$  input variables
  - Eg) 3 to 8 line decoder

**Table 4-6**  
*Truth Table of a 3-to-8-Line Decoder*

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


 


Fig. 4-18 3-to-8-Line Decoder
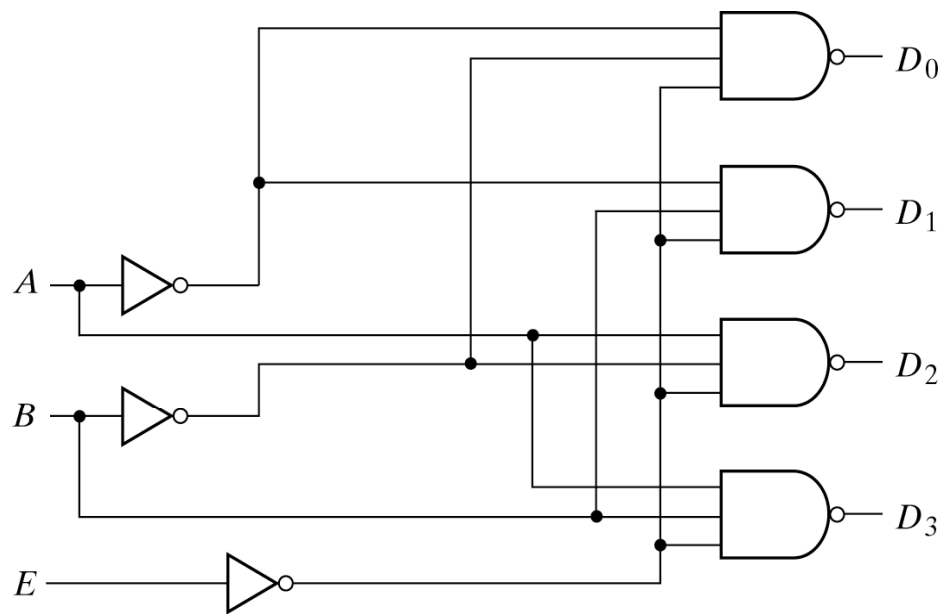
## 4.9 Decoders

- 2 to 4 line decoder with Enable input
  - Control circuit operation by E



(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

## 4.9 Decoders

- Decoders with enable inputs can be a larger decoder circuit

Eg) 4x16 decoder by two 3x8 decoders

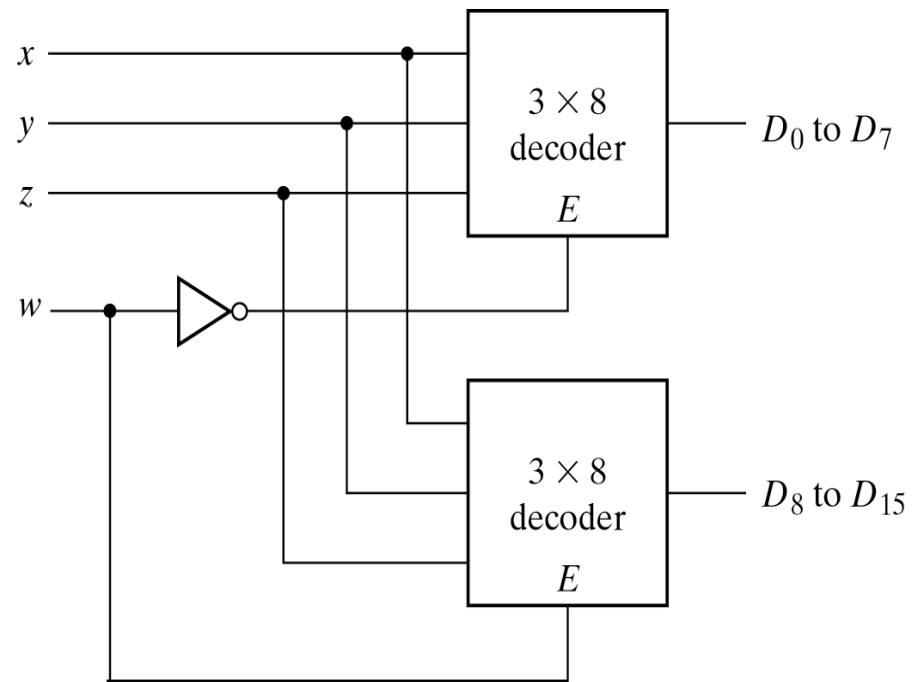


Fig. 4-20  $4 \times 16$  Decoder Constructed with Two  $3 \times 8$  Decoders

## 4.9 Decoders - Combinational logic implementation

- Combinational logic implementation
  - Any combinational circuit can be implemented with line decoder and OR gates
  - Eg) full adder

**Table 4-4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

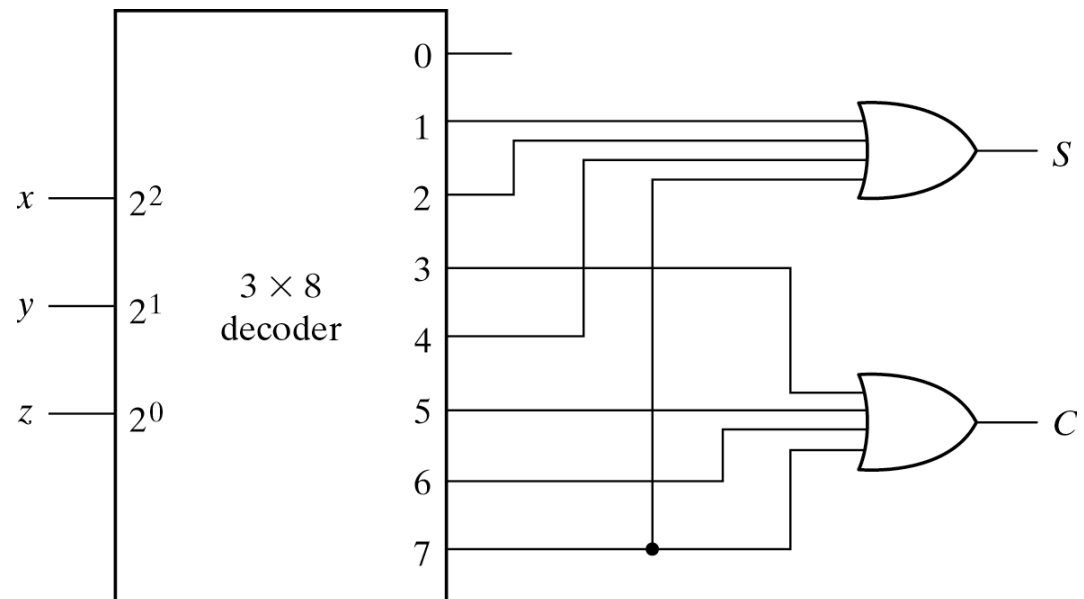


Fig. 4-21 Implementation of a Full Adder with a Decoder

## 4.10 Encoders

- Inverse operation of a decoder
- Generate  $n$  outputs of  $2^n$  input values
  - Eg) octal to binary encoder

decode  
 $2^n$   $n$

**Table 4-7**  
*Truth Table of Octal-to-Binary Encoder*

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



## 4.10 Encoders - Priority encoder

- Problem happens two or more inputs equal to 1 at the same time
- Give a priority function to circuit

**Table 4-8**  
*Truth Table of a Priority Encoder*

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	$X$	$X$	0
1	0	0	0	0	0	1
$X$	1	0	0	0	1	1
$X$	$X$	1	0	1	0	1
$X$	$X$	$X$	1	1	1	1

(x100 means 0100, 1100)

 


Fig. 4-22 Maps for a Priority Encoder

## 4.11 Multiplexers


- Select a binary information from many input lines
- Selection is controlled by a set of selection lines
- $2^n$  input lines have  $n$  selection lines

## 4.11 Multiplexers

### 4 to 1 line multiplexer

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

 

(a) Logic diagram

## 4.11 Multiplexers

### • Quadruple 2 to 1 line multiplexer

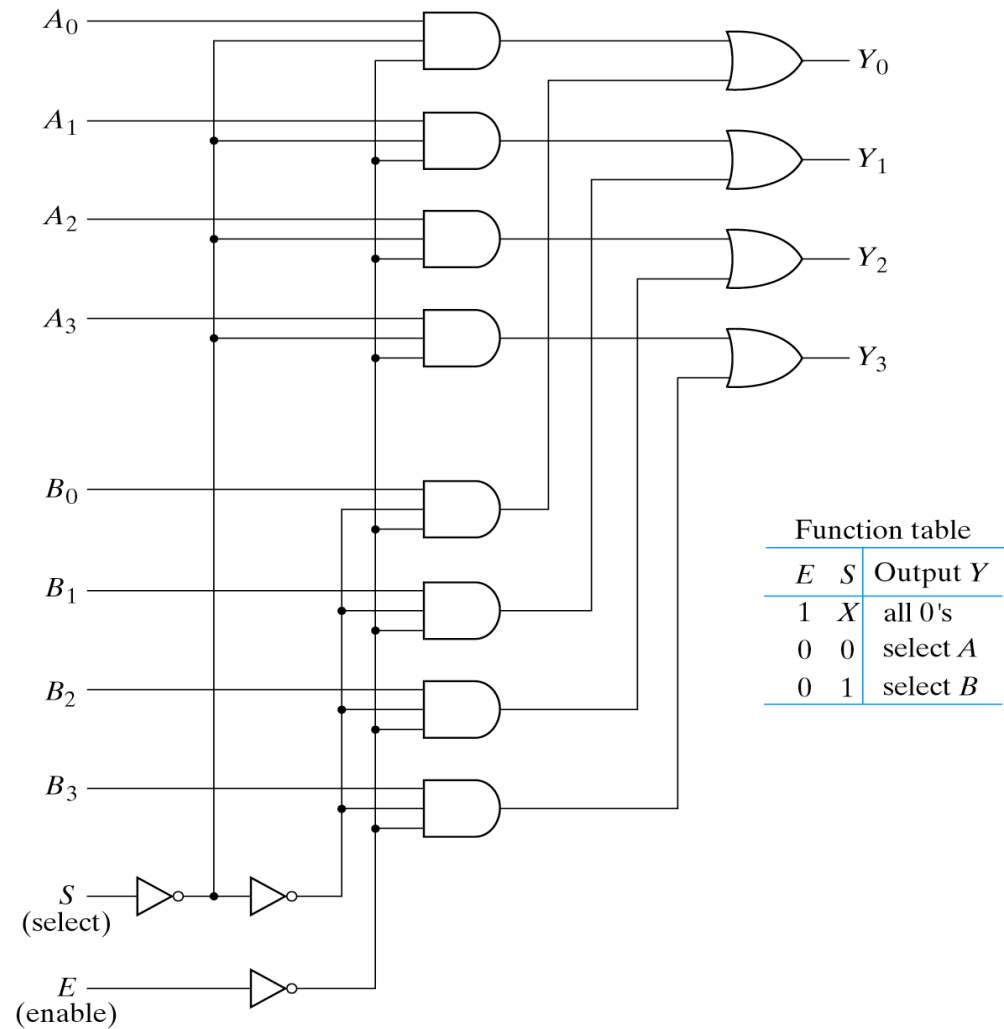



Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

## 4.11 Multiplexers - Boolean function implementation

- Boolean function implementation
  - Minterms of function are generated in a MUX
  - $n$  input variables,  $n-1$  selection input

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

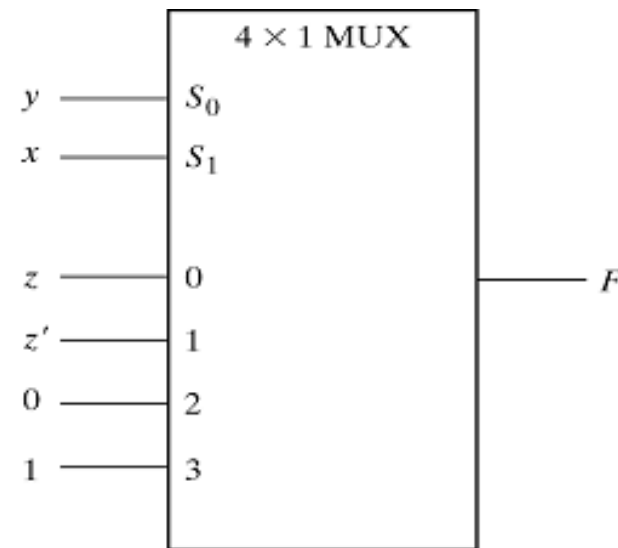

(b) Multiplexer implementation

$$F = xy + yz' + x'y'z$$

## 4.11 Multiplexers - Three-state gates

- Three-state gates
  - Logic 1, 0 and *high-impedance*
  - *High-impedance* behaves like an open circuit


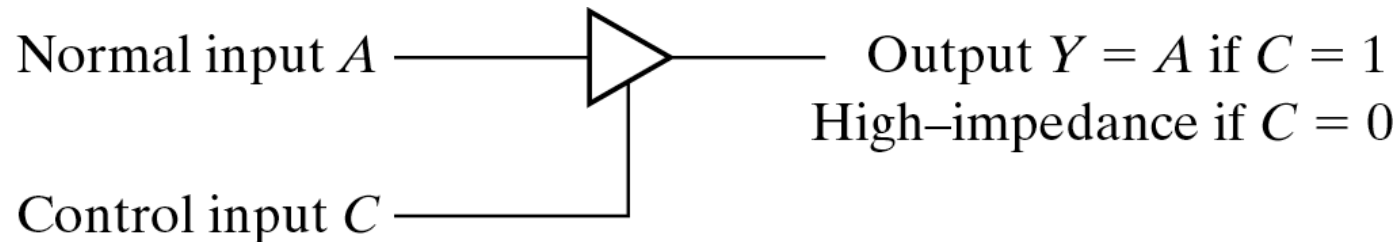



Fig. 4-29 Graphic Symbol for a Three-State Buffer

## 4.11 Multiplexers
 
### • Multiplexers with three-state gates



(a) 2-to-1- line mux

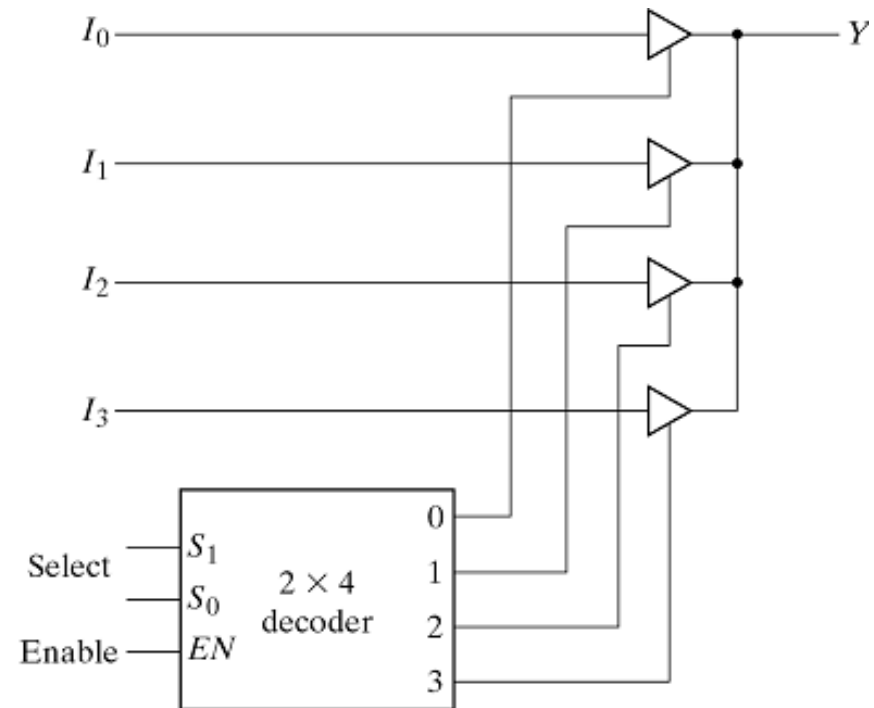

(b) 4 - to - 1 line mux

Fig. 4-30 Multiplexers with Three-State Gates


## 4.12 HDL for combinational circuit

- Modeling techniques:
  - Gate level modeling
    - Instantiation of gates and user defined modules
  - Dataflow modeling
    - Using continuous assignment statements-***assign***
  - Behavioral modeling
    - Using procedural assignment statements-***always***


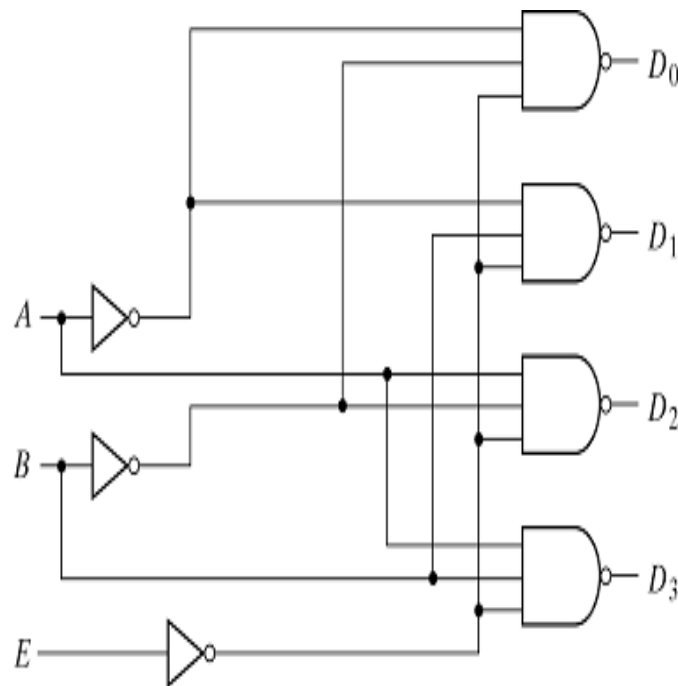
## 4.12 HDL for combinational circuit - Gate-level modeling

- Circuit is specified by its gates and their interconnection



HDL Example 4-1


//Gate-level description of a 2-to-4-line decoder  
//Figure 4-19

```
module decoder_g1 (A,B,E,D);  
  input A,B,E;  
  output [0:3]D;  
  wire Anot,Bnot,Enot;  
  not  
    n1 (Anot,A),  
    n2 (Bnot,B),  
    n3 (Enot,E);  
  nand  
    n4 (D[0],Anot,Bnot,Enot),  
    n5 (D[1],Anot,B,Enot),  
    n6 (D[2],A,Bnot,Enot),  
    n7 (D[3],A,B,Enot);  
endmodule
```

## 4.12 HDL for combinational circuit - Gate-level modeling
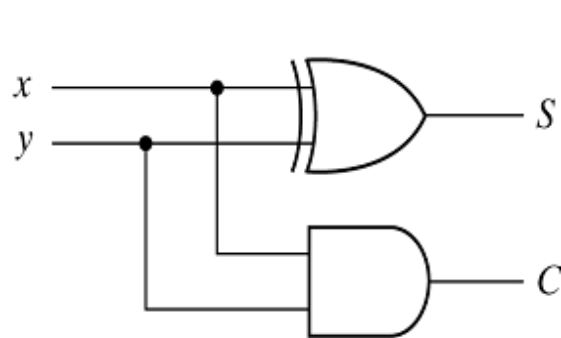
### Instantiation

```
module halfadder (S,C,x,y);  
    input x,y;  
    output S,C;  
    //Instantiate primitive gates  
    xor (S,x,y);  
    and (C,x,y);  
endmodule
```



```
module fulladder (S,C,x,y,z);  
    input x,y,z;  
    output S,C;  
    wire S1,D1,D2;  
    //Instantiate the halfadder  
    halfadder HA1 (S1,D1,x,y),  
               HA2 (S,D2,S1,z);  
    or g1 (C,D2,D1);  
endmodule
```

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

## 4.12 HDL for combinational circuit - Gate-level modeling

### Instantiation in 4-bit adder

```
module _4bit_adder (S,C4,A,B,C0);  
    input [3:0] A,B;  
    input C0;  
    output [3:0] S;  
    output C4;  
    wire C1,C2,C3; //Intermediate carries  
    //Instantiate the fulladder  
    fulladder FA0 (S[0],C1,A[0],B[0],C0),  
                FA1 (S[1],C2,A[1],B[1],C1),  
                FA2 (S[2],C3,A[2],B[2],C2),  
                FA3 (S[3],C4,A[3],B[3],C3);  
endmodule
```

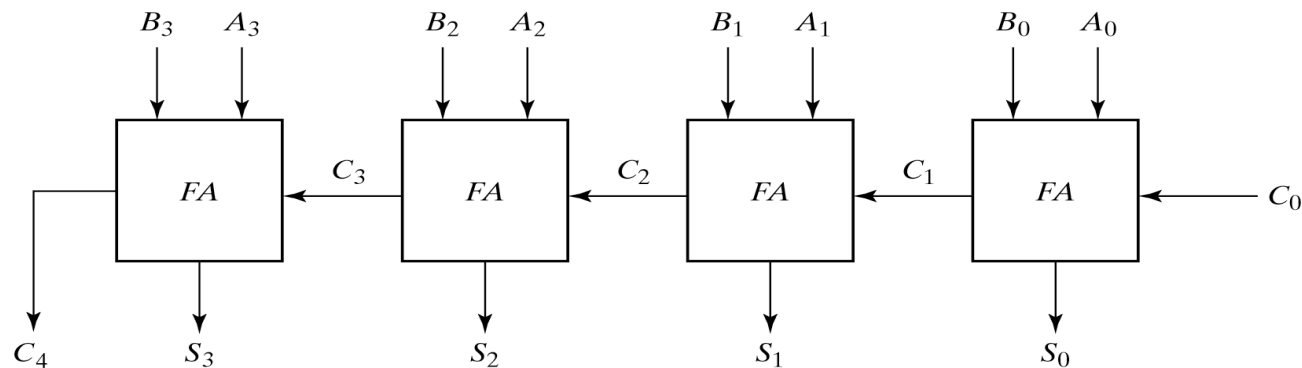


Fig. 4-9 4-Bit Adder

## 4.12 HDL for combinational circuit - 3 State Gate

## 4.12 HDL for combinational circuit - Dataflow modeling

- Assign a value to a net by using operands and operators

eg)  $J=01, K=10$  can be  
 $\{J, K\}=0110$

$\text{out} = x ? A : B$  means  
 $\text{out} = A$ , if  $x$  is true  
 $= B$ , if  $x$  is false


**Table 4-10**  
*Verilog HDL Operators*

Symbol	Operation
+	binary addition
-	binary subtraction
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~	bit-wise NOT
==	equality
>	greater than
<	less than
{ }	concatenation
?:	conditional

## 4.12 HDL for combinational circuit - Dataflow modeling

### ● Assignment

- 2-to-4 line decoder

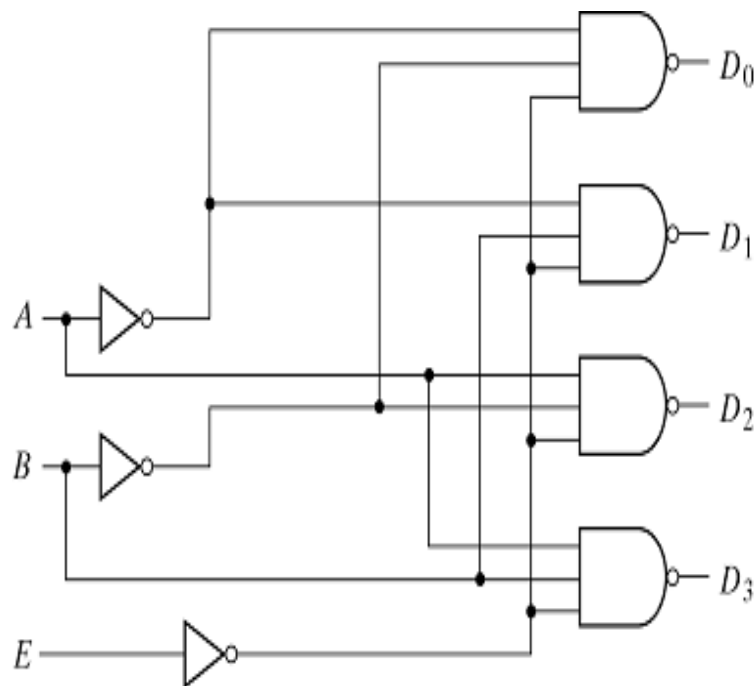

### HDL Example 4-3

//Dataflow description of a 2-to-4-line decoder  
//See Fig. 4-19

```
module decoder_df (A,B,E,D);  
    input A,B,E;  
    output [0:3] D;  
    assign D[0] = ~(~A & ~B & ~E),  
           D[1] = ~(~A & B & ~E),  
           D[2] = ~(A & ~B & ~E),  
           D[3] = ~(A & B & ~E);  
endmodule
```

## 4.12 HDL for combinational circuit - Dataflow modeling

### ● Assignment - 4-bit adder

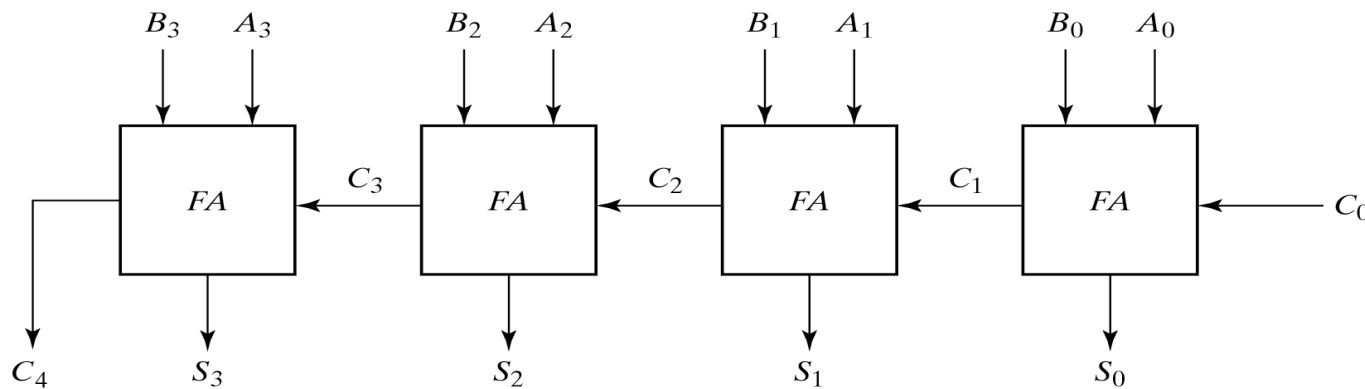


Fig. 4-9 4-Bit Adder

### HDL Example 4-4

```
//Dataflow description of 4-bit adder
module binary_adder (A,B,Cin,SUM,Cout);
    input [3:0] A,B;
    input Cin;
    output [3:0] SUM;
    output Cout;
    assign {Cout,SUM} = A + B + Cin;
endmodule
```

## 4.12 HDL for combinational circuit - Behavioral modeling

- Use procedural assignment statement, ***always***

- Target output must be the *reg* data type

Eg) 4 to 1 line mux

```
module mux4x1_bh (i0,i1,i2,i3,select,y);  
    input i0,i1,i2,i3;  
    input [1:0] select;  
    output y;  
    reg y;  
    always @ (i0 or i1 or i2 or i3 or select)  
        case (select)  
            2'b00: y = i0;  
            2'b01: y = i1;  
            2'b10: y = i2;  
            2'b11: y = i3;  
        endcase  
endmodule
```



## 4.12 HDL for combinational circuit - Writing a simple test bench

- Test bench : Applying stimulus to test HDL and observe its response
- **reg** - inputs , **wire** - outputs

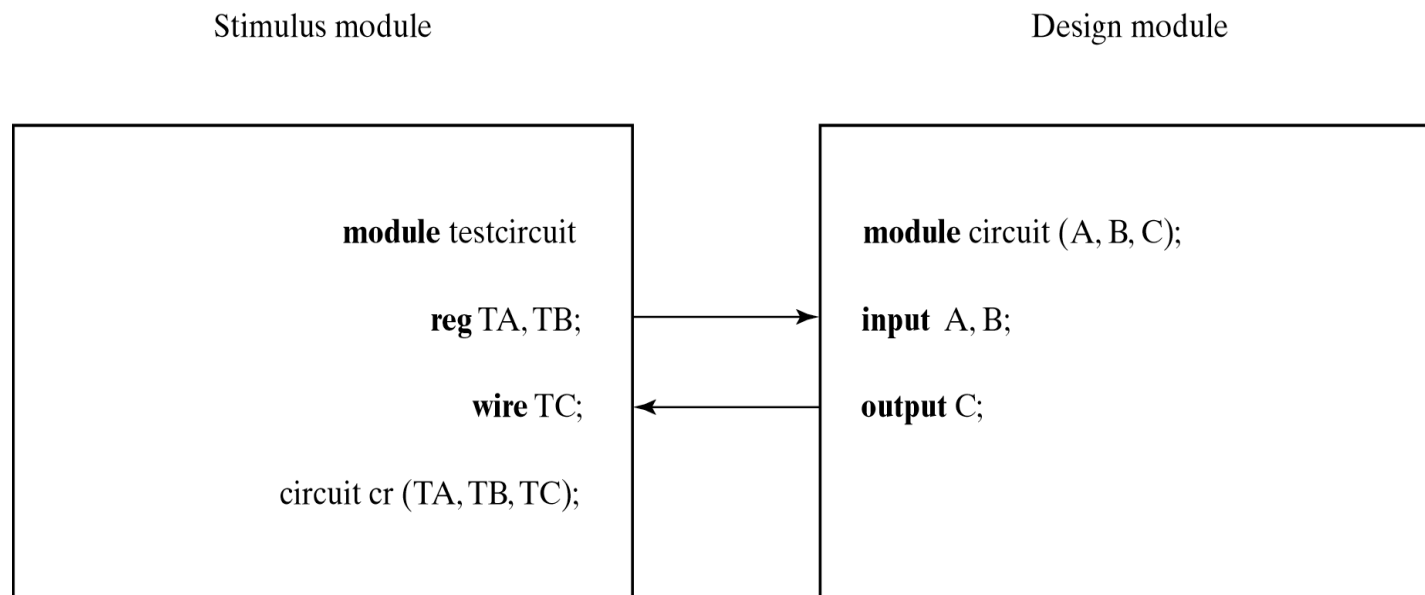



Fig. 4-33 Stimulus and Design Modules Interaction

## 4.12 HDL for combinational circuit - Writing a simple test bench

- System tasks : keywords that can display various outputs (begin with \$)
- \$display , \$write , \$monitor , \$time , \$finish
- Format of system tasks
  - Task name(format specification,argument list);
  - Eg) \$monitor(%d %b %b, C,A,B);

## 4.12 HDL for combinational circuit - Writing a simple test bench

### ● Example of test bench

 

```
//Stimulus for mux2x1_df.
module testmux;
    reg TA,TB,TS; //inputs for mux
    wire Y;       //output from mux
    mux2x1_df mx (TA,TB,TS,Y); // instantiate mux
    initial
        begin
            TS = 1; TA = 0; TB = 1;
            #10 TA = 1; TB = 0;
            #10 TS = 0;
            #10 TA = 0; TB = 1;
        end
    initial
        $monitor("select = %b A = %b B = %b OUT = %b time = %0d",
            TS, TA, TB, Y, $time);
endmodule

//Dataflow description of 2-to-1-line multiplexer
//from Example 4-6
module mux2x1_df (A,B,select,OUT);
    input A,B,select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
```